

MAS836 – Sensor Technologies for Interactive Environments

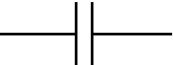


Lecture 2 – Analog Conditioning Electronics, Pt. 2

Reading...

- Horowitz and Hill
 - Finish Chapter 1, read Chapters 4&5
- Fraden
 - Interface Electronic Circuits Chapter (Chapter 6 of last edition)

Reactive Impedance

- The Capacitor 
 - Adds in parallel like resistors add in series
 - Reciprocal-adds in series like resistors add in parallel
- Impedance of capacitor = $-j/\omega C = -j/(2\pi f C)$ *C in Farads*
 - Pass AC, block DC
 - Capacitor current: $I_C = C dV/dt$
- Impedance of inductor = $j\omega L = j(2\pi f L)$ *L in Henries*
 - Block AC, pass DC
 - Inductor Voltage: $V = L dI/dt$



Passive RC Filters

- Passive LP Filter: RC network: $f_c = 1/(2\pi RC)$

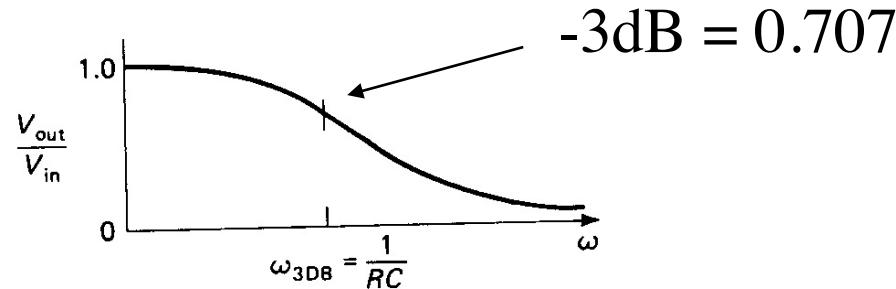
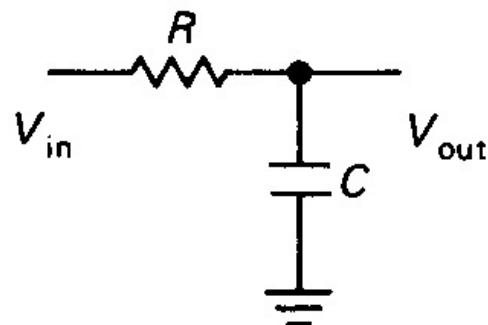


Figure 1.59. Frequency response of low-pass filter.

- Passive HP filter: RC network: $f_c = 1/(2\pi RC)$

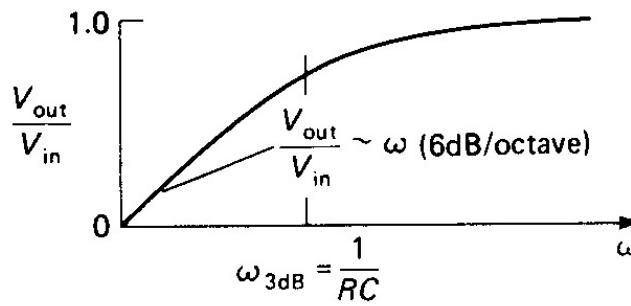
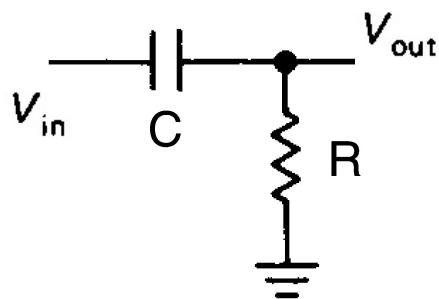



Figure 1.55. Frequency response of high-pass filter.

Note - To take the magnitude of a complex impedance, add the real and imaginary parts in *quadrature*

L/C Reciprocal Action


- If a capacitor is replaced with an inductor, the filter flips its nature
 - A capacitive highpass becomes an inductive lowpass

Passive RC Filter Rolloff

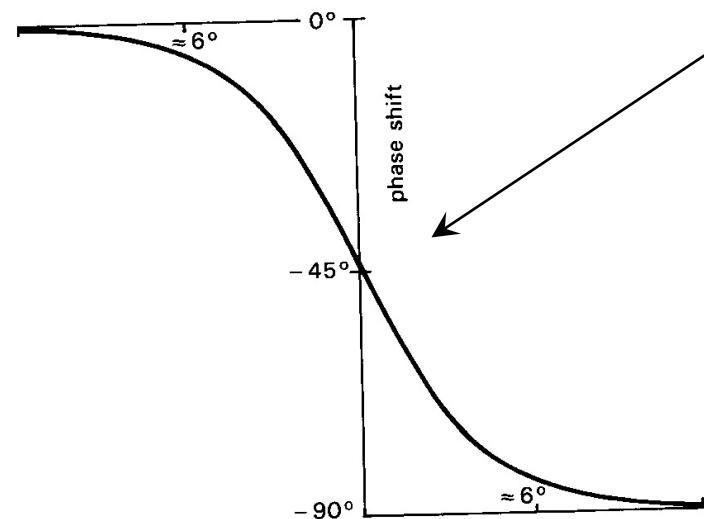

Phase between input and output
is 45° at cutoff

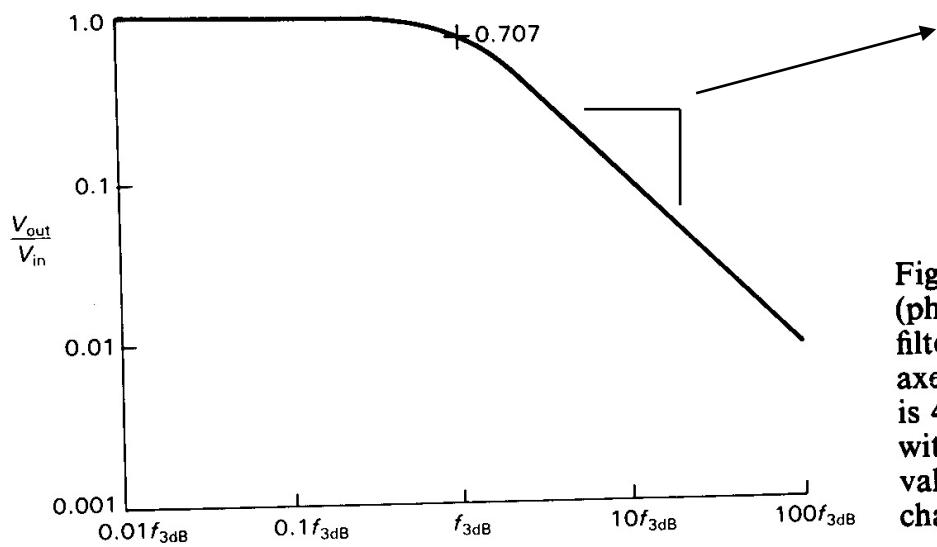Bode Plot:
Freq. Response as a log-log plot





Rolloff is 6 dB per Octave (2x)
20 dB per Decade (10x)

Figure 1.60. Frequency response (phase and amplitude) of low-pass filter, plotted on logarithmic axes. Note that the phase shift is 45° at the 3dB point and is within 6° of its asymptotic value for a decade of frequency change.

Passive RLC Filters

- Resonant parallel RLC bandpass filters

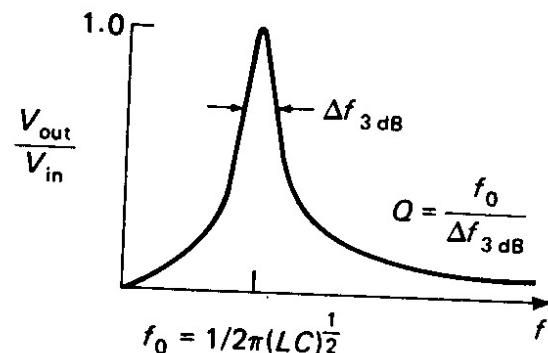
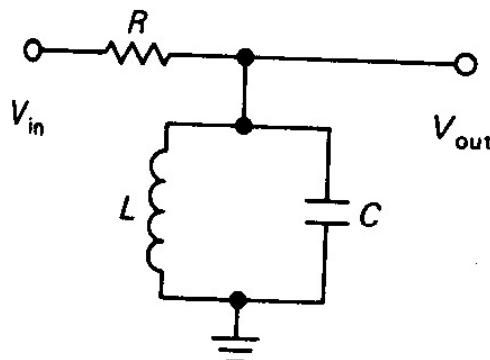


$$Q = \omega_0 RC$$

$$= f_0 / \Delta f_{3 \text{ dB}}$$

$Z_{\text{LC}} \rightarrow \infty @ f_0$

- Resonant series RLC notch filters

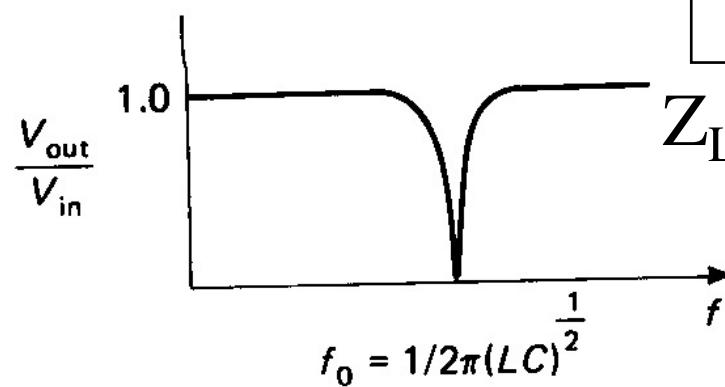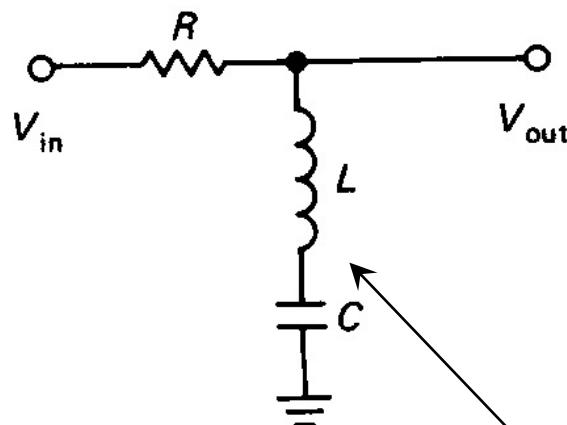

$$Q = \omega_0(L/R)$$

$$= f_0 / \Delta f_{3 \text{ dB}}$$

$Z_{\text{LC}} \rightarrow 0 @ f_0$

Voltage here is pumped up




Active Filters

- The Differentiator
- The Active High-Pass Filter
- Principle of Feedback Inversion
- The Integrator
- The Leaky Integrator (LP filter)
- Buffered Passive Second-Order Filter
- Sallen-Key (or VCVS) LP, HP, BP filters
- Single-OpAmp VCVS BP filter


The Differentiator

The Differentiator

i_f

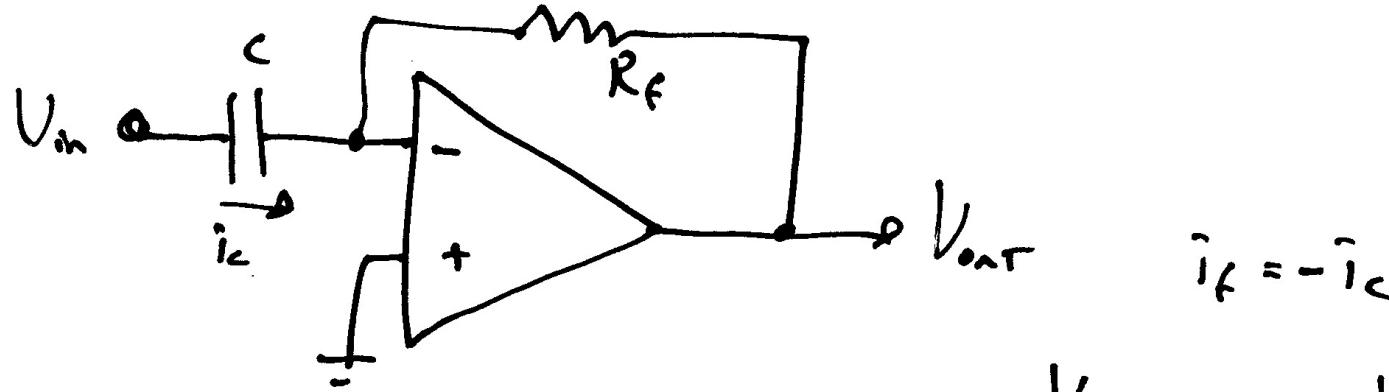


$$i_f = -i_C$$

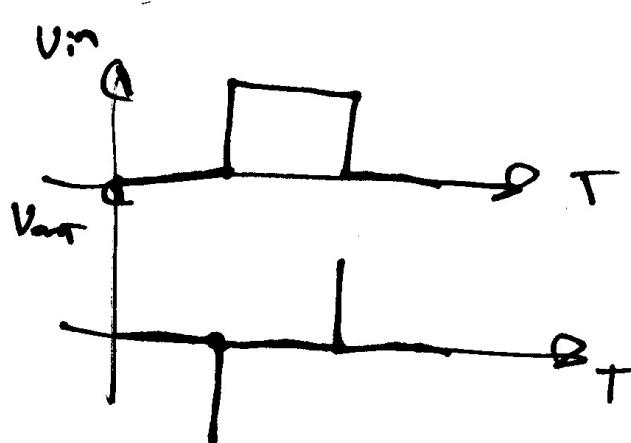

$$\frac{V_{out}}{R_f} = -C \frac{dV_{in}}{dT}$$

$$V_{out} = -R_f C \frac{dV_{in}}{dT}$$



The First-Order Active High Pass Filter

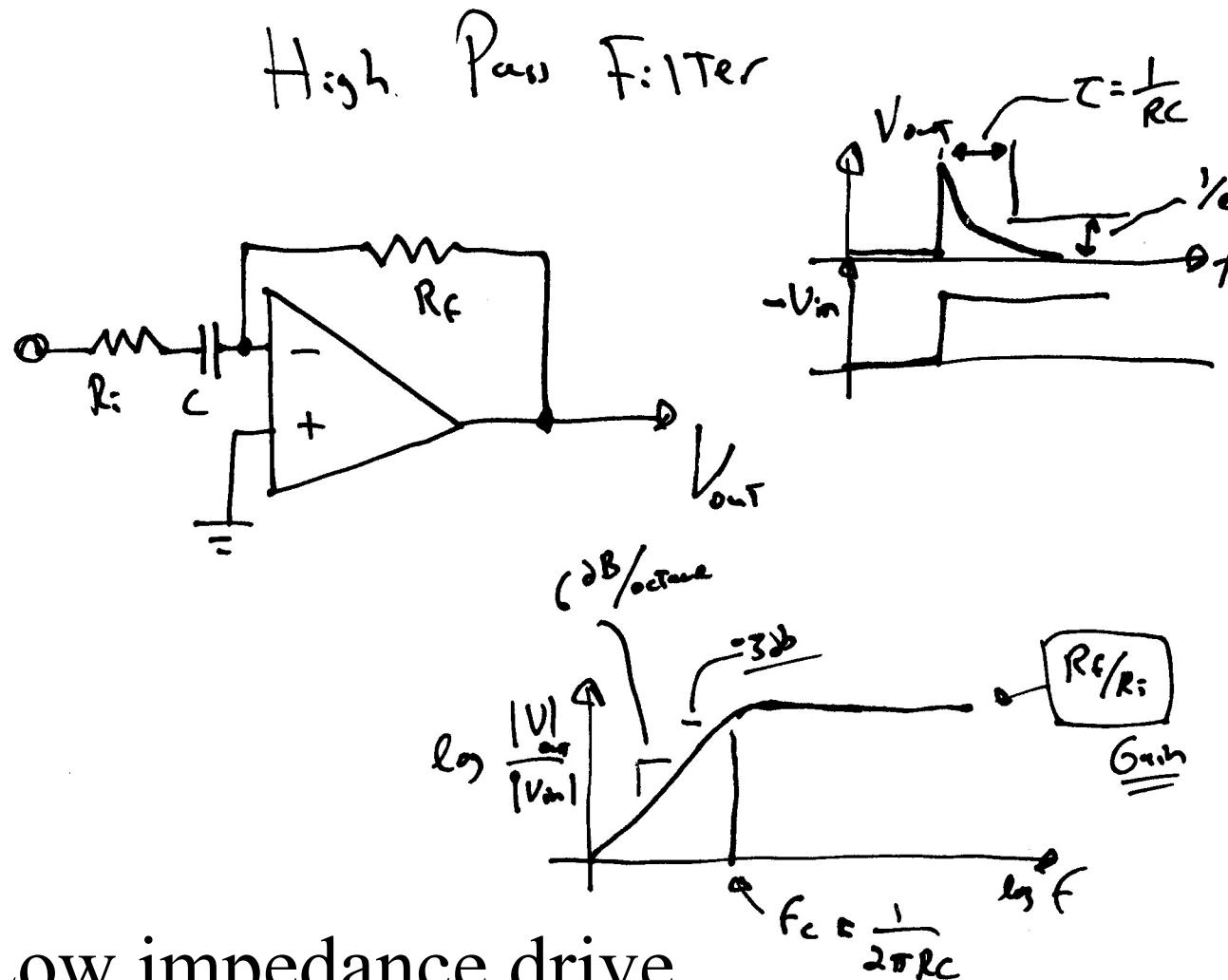

- Low impedance drive
- Voltage gain via R_f/R_i

The Integrator

The Integrator

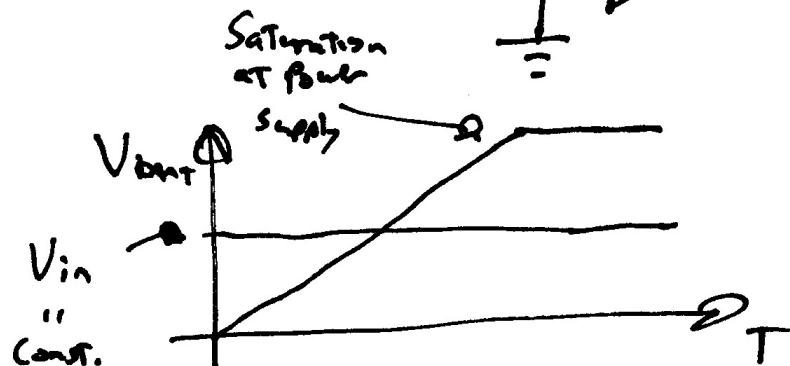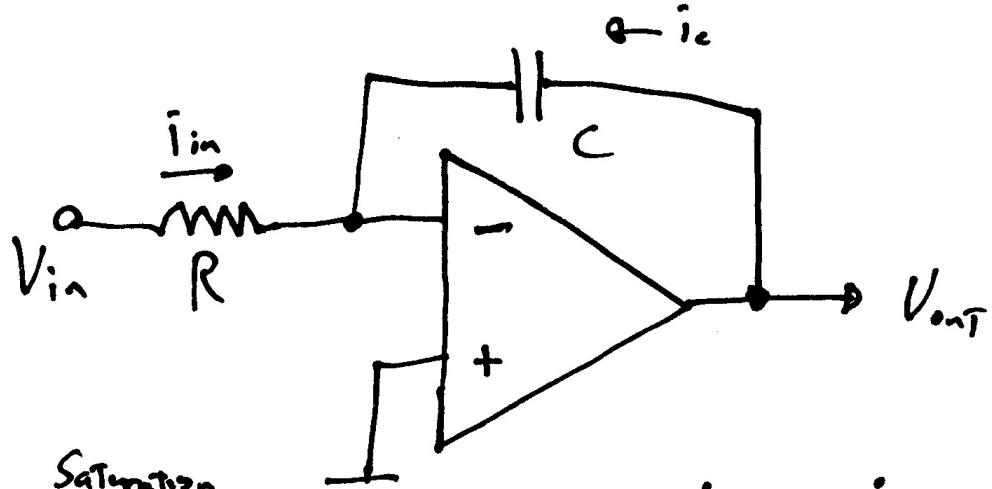

Saturates at rail!!



$$Z_C = \frac{1}{j\omega C}$$

$$i_C = C \frac{dV}{dT}$$

$$i_C = -i_{in} \Rightarrow C \frac{dV_{out}}{dT} = -\frac{V_{in}}{R}$$

$$\frac{dV_{out}}{dT} = -\frac{V_{in}}{RC} \Rightarrow V_{out} = \underline{\underline{\frac{1}{RC} \int V_{in} dt}}$$



Integrator with Reset Switch

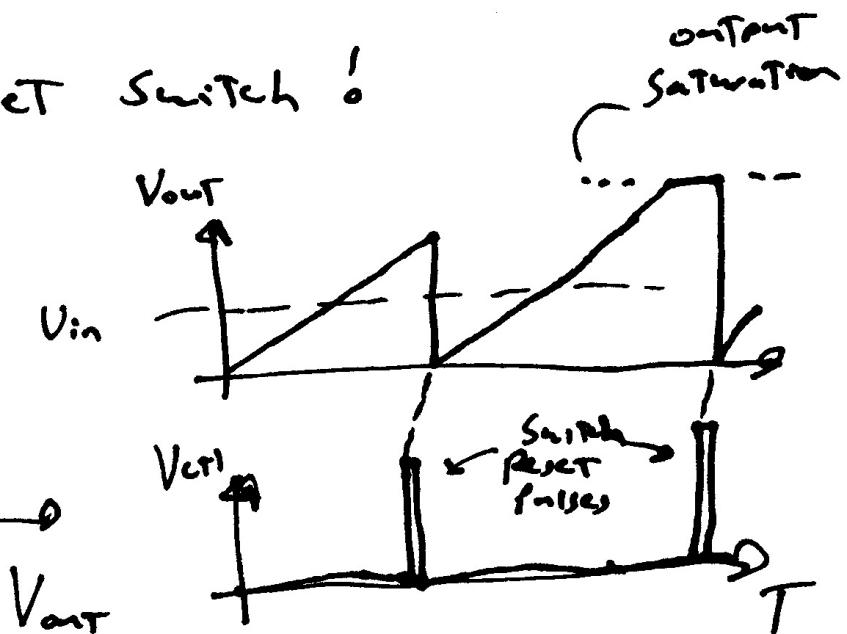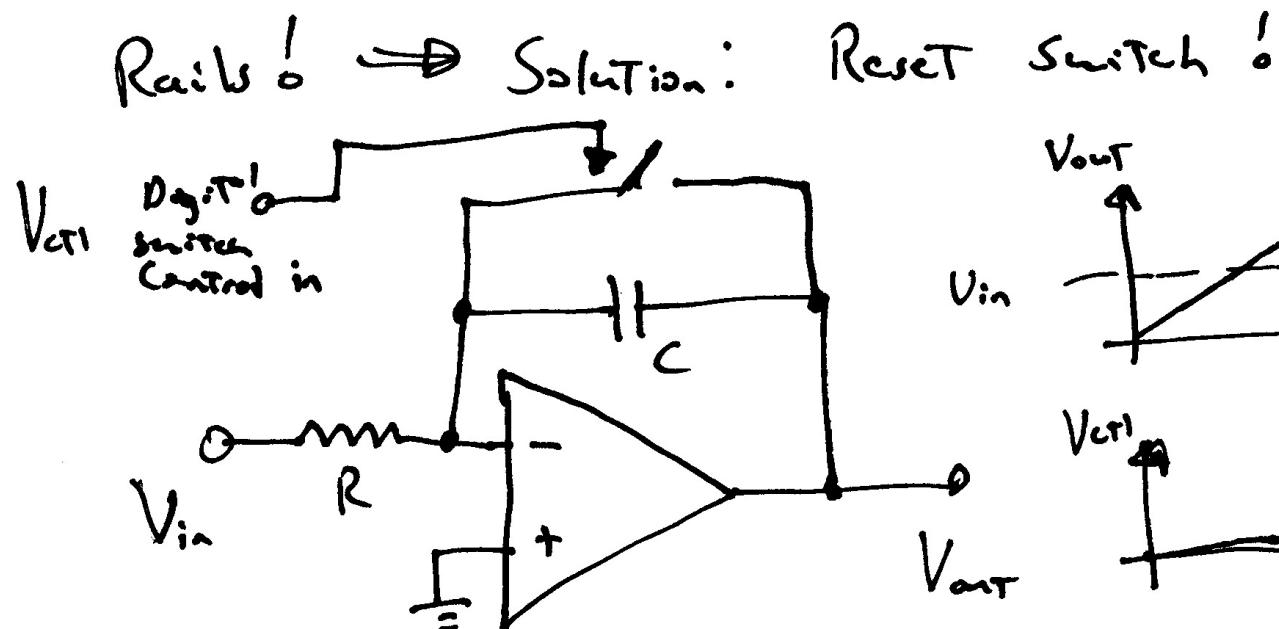

- Electronic switch in feedback forces output to ground when closed
 - Discharges capacitor
 - Resets Integrator!


The First-Order Active Low Pass Filter

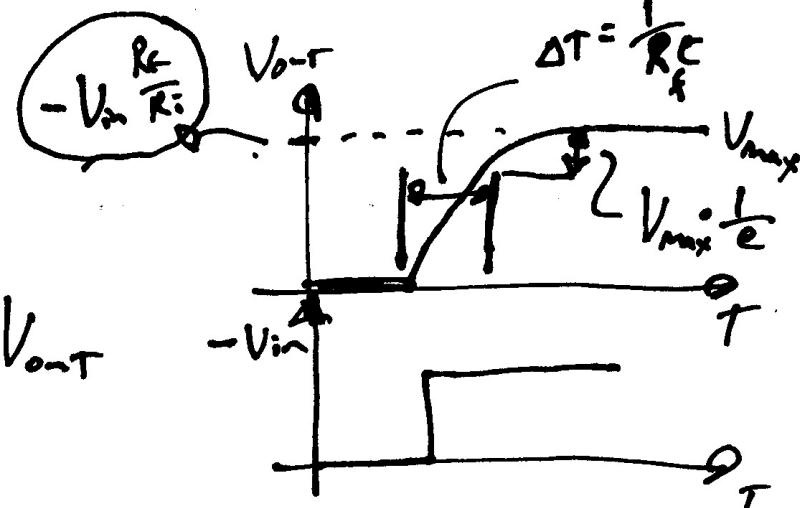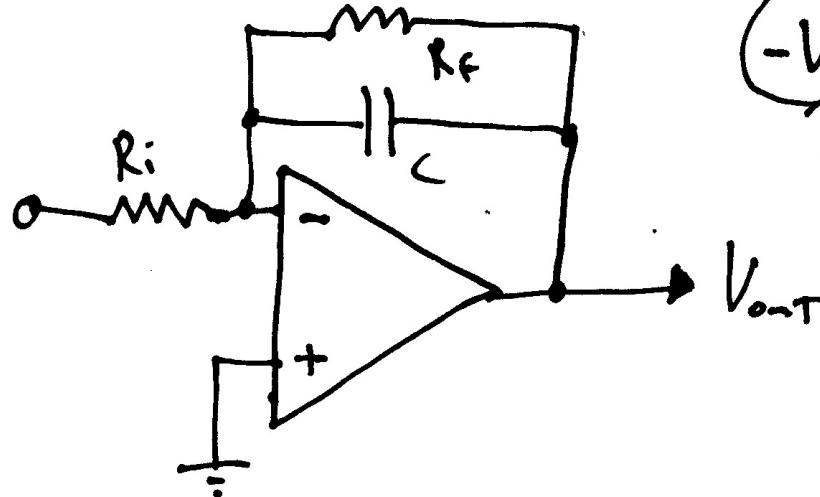The Leaky Integrator \rightarrow Low Pass Filter




Low impedance
output !!

Voltage gain 1/6

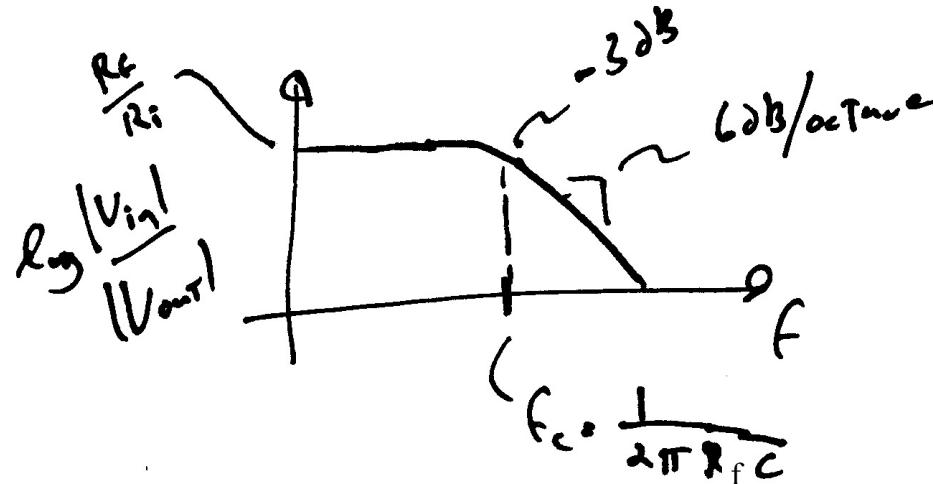


The Band-Select Filter

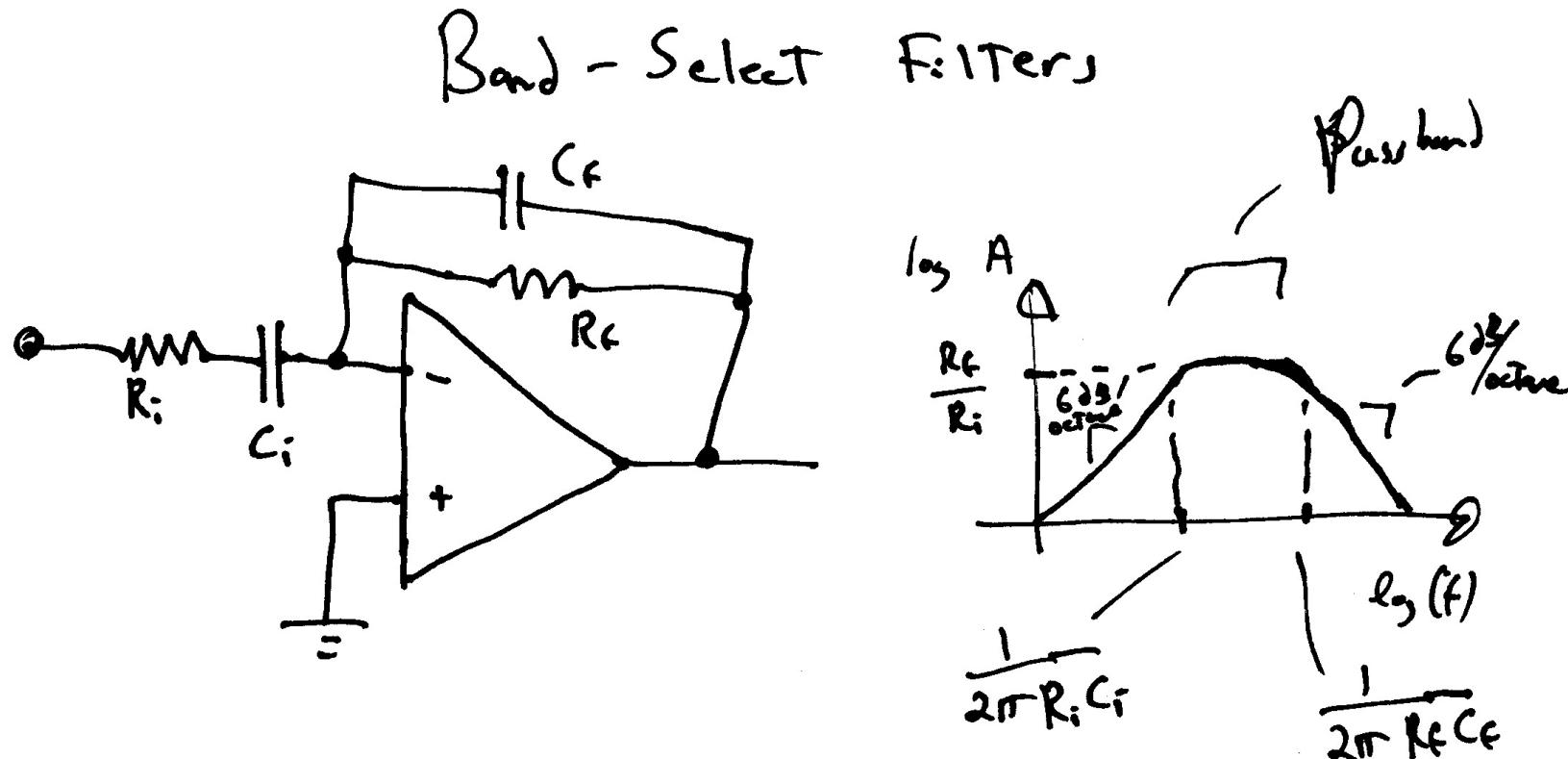

- Cascaded high and low pass filters
 - Always follow high-pass with low-pass (noise)
 - Low-Pass cutoff needs to be below high-pass cutoff!
 - No Q, first-order rolloffs

Sallen-Key Filters – Ref. Active Filter Cookbook

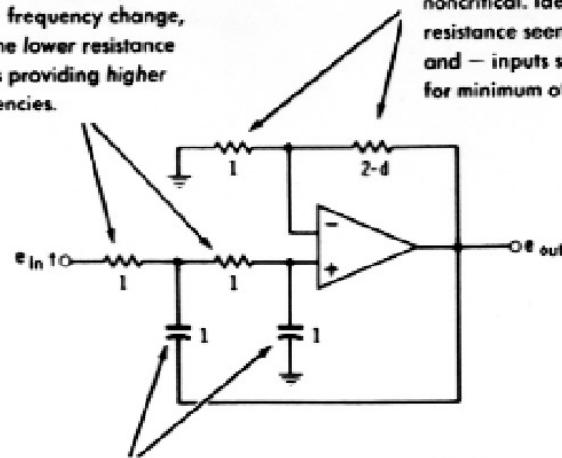Change **FREQUENCY** smoothly by varying these two resistors. Keep both these resistors identical in value at all times. A 10:1 resistance change provides a 10:1 frequency change, with the lower resistance values providing higher frequencies.



Change **FREQUENCY** in steps by switching these capacitors. Keep both capacitors identical in value at all times. Doubling the capacitors halves the frequency and vice versa.

† must return to ground via low-impedance dc path.

Fig. 6-8. Adjusting or tuning the equal-component-value, Sallen-Key, second-order, low-pass section.


Change **DAMPING** by using these two resistors to set the amplifier gain at $(3 - d)$. This is done by making the right resistor $2 - d$ times larger than the left one. The absolute values of these resistors are noncritical. Ideally the resistance seen on the + and - inputs should be equal for minimum offset.

GAIN of this circuit is fixed at $3 - d$ or roughly 2:1 (+6 decibels). Adjust signal levels elsewhere in the system.

(Circuit becomes high-pass by switching positions of frequency-determining resistors and capacitors.)

Change **FREQUENCY** in steps by switching these capacitors. Keep both capacitors identical in value at all times. A 10:1 capacitance change provides a 10:1 frequency change, with the lower C values producing higher frequencies.

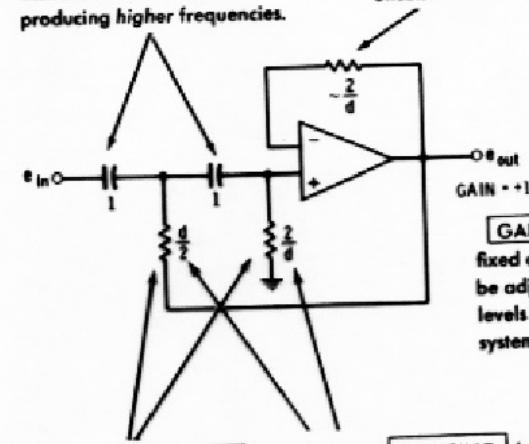This resistor is not critical and may be replaced with a short for noncritical circuits. Ideally the dc resistance on + and - inputs should be equal for minimum offset.




Change **FREQUENCY** smoothly by varying these resistors. Keep the right resistor $4/d^2$ times as large as the left one at all times. Doubling resistance halves frequency and vice versa.

Adjust **DAMPING** by changing the ratio of these two resistors while keeping their product constant.

(There is no reasonable way to convert this circuit to low-pass or bandpass with simple switching.)

Fig. 8-5. Adjusting or tuning the unity-gain, Sallen-Key, second-order high-pass section.

Multiple Feedback Bandpass

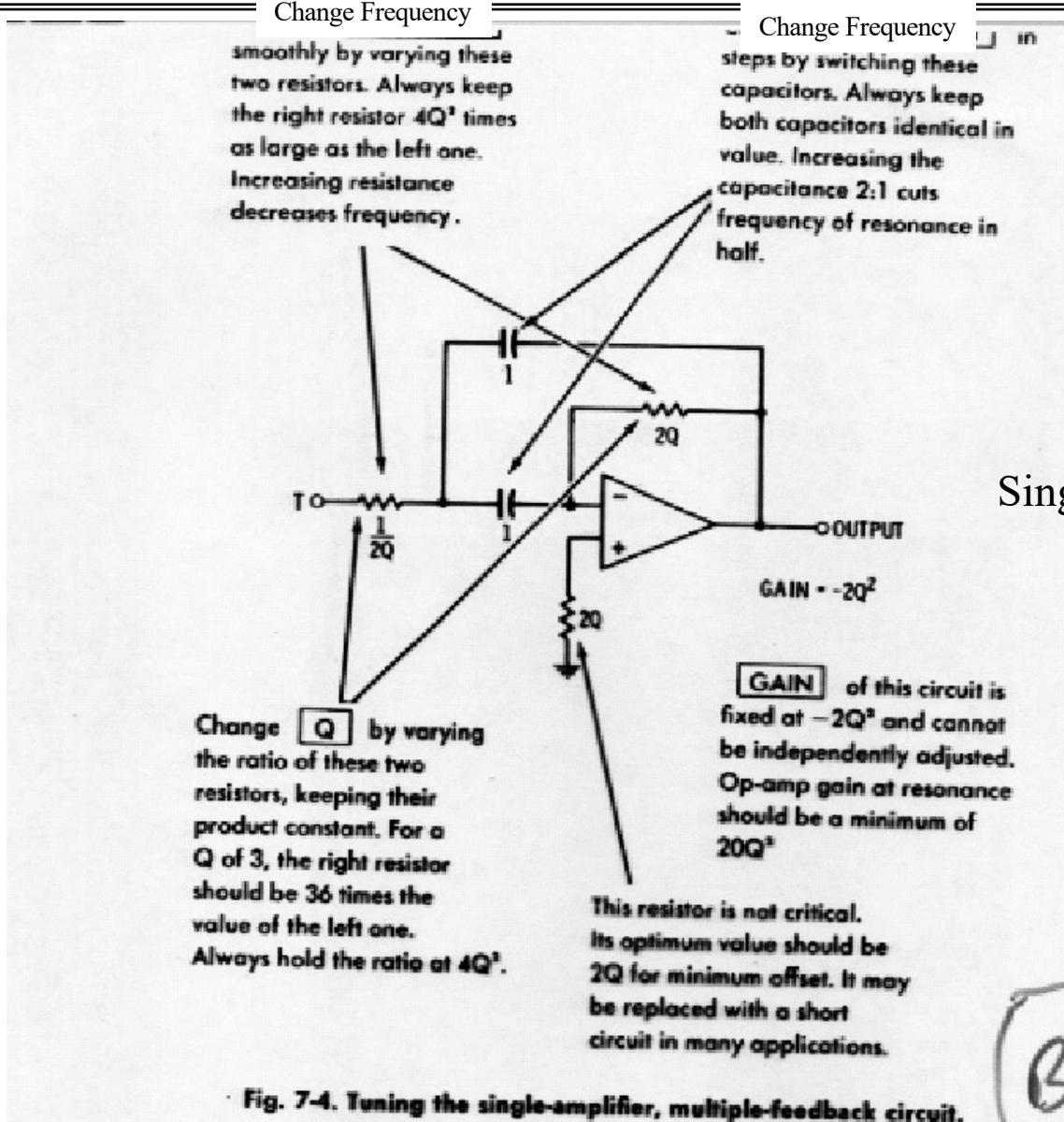

Single-OpAmp VCVS BP filter

Good for Q up to 10 or so

(B)

Low Pass Filter Responses

Best-Time-Delay Filter—Sometimes called a *Bessel* filter. This one has the best possible time delay and overshoot response, but it has a droopy passband and very gradual initial falloff.

Compromise Filter—Often called a *Paynter* or *transitional Thompson-Butterworth* filter. It has a somewhat flatter passband and initially falls off moderately faster than the best-time-delay filter, with only moderately poorer overshoot characteristics.

Flattest-Amplitude Filter—This is the *Butterworth* filter and has the flattest passband you can possibly provide combined with a moderately fast initial falloff and reasonable overshoot. The overshoot characteristics appear in Fig. 4-10. *The Butterworth is often the best overall filter choice.* It also has a characteristic that sets all cascaded sections to the same frequency, which makes voltage control and other wide-range tuning somewhat easier.

Slight-Dips Filter—This is the first of the *Chebyshev filters*. It has a slight peaking or ripple in the passband, a fast initial falloff, and a

transient response only slightly worse than the flattest-amplitude filter. The ripple depends on the order and varies from 0.3 dB for the second-order response down to .01 dB at the sixth-order.

One-dB-Dips Filter—This is another Chebyshev filter. It has 1 dB of passband ripple. The ripple peaks and troughs are constant in amplitude, but you get more of them as the order increases. They tend to crowd together near the cutoff frequency, particularly when viewed on a log response plot.

Two-dB-Dips Filter—Another Chebyshev filter. The 2-dB ripple gives faster initial stopband falloff and progressively poorer transient and overshoot characteristics.

Three-dB-Dips Filter—This final Chebyshev filter offers the fastest initial falloff you can possibly get in a filter with acceptable passband lumps and continually increasing attenuation in the stopband.

Response set by adjusting R's and C's


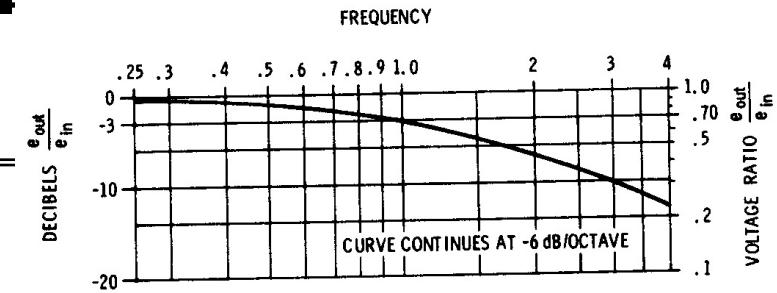


Fig. 4-4. First-order low-pass response.

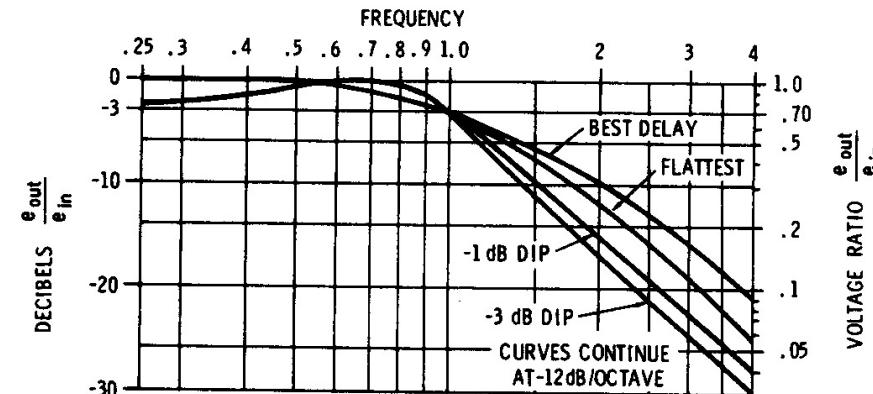

(A) Response curves.

A second-order filter is built with a single second-order section. Its ultimate attenuation rate is -12 dB/octave .

For a cutoff (-3 dB) frequency of f , the section parameters are:

Filter Type	Second-Order Section	
	Frequency	Damping
Best Delay	1.274 f	1.732
Compromise	1.128 f	1.564
Flattest Amp	1.000 f	1.414
Slight Dip	0.929 f	1.216
1-Decibel Dip	0.863 f	1.045
2-Decibel Dip	0.852 f	0.895
3-Decibel Dip	0.841 f	0.767

Zero frequency attenuation is 0 decibels for first four filter types, -1 dB for 1-dB dip, -2 dB for 2-dB dip, and -3 dB for 3-dB dip filter types.

NOTE—Values on this chart valid only for second-order filters. See other charts for suitable values when sections are cascaded.

Or just run an applet...

- Analog Devices, TI, etc.


<http://www.analog.com/designtools/en/filterwizard/>

[http://webench.ti.com/webench5/power/webench5.cgi?
app=filterarchitect&filterType=Lowpass](http://webench.ti.com/webench5/power/webench5.cgi?app=filterarchitect&filterType=Lowpass)

Most relevant to class:

<http://sim.okawa-denshi.jp/en/Fkeisan.htm>

State Variable Filter

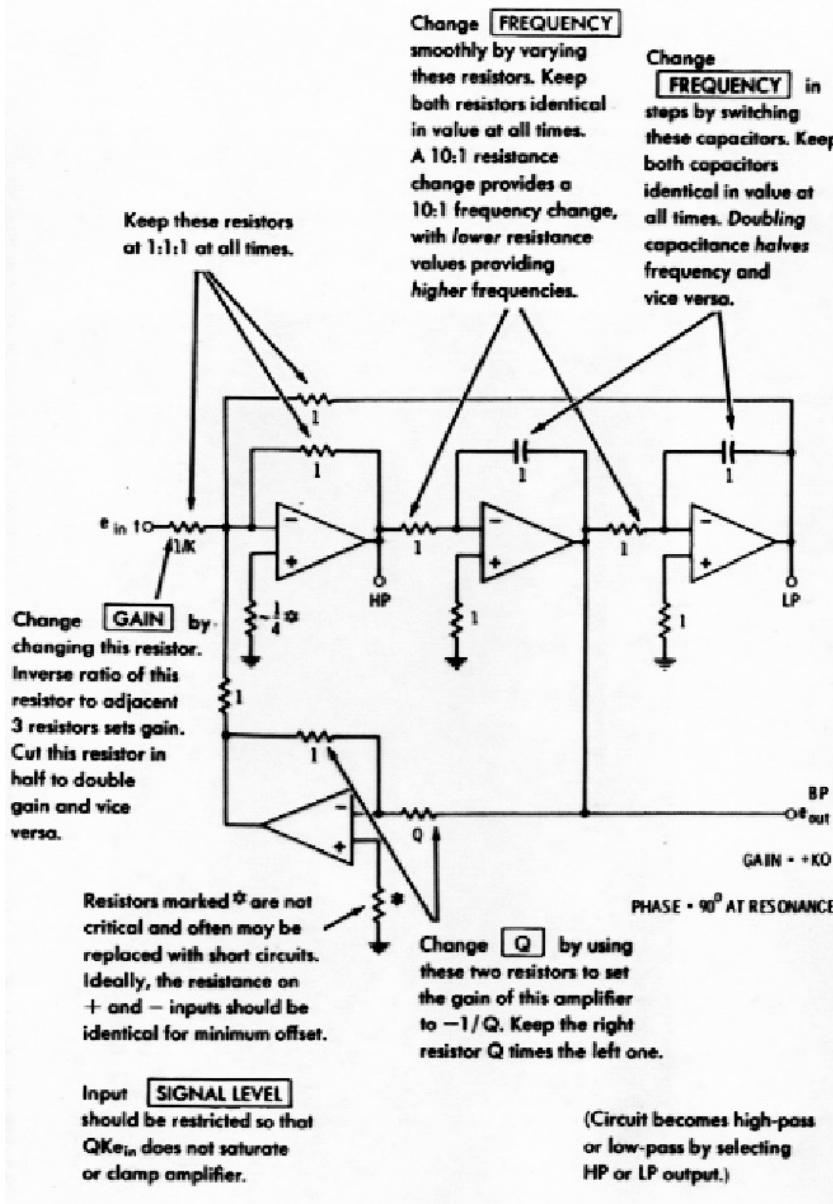


- Very high Q possible (e.g., 500!)
- Simultaneous outputs
- Other varieties (BiQuad, etc.)
- Can make frequency-tunable w. multipliers substituted for coupling resistors
 - (VCF)
- Switched-Capacitor Filter Intro.

The State Variable Filter


STATE Variable VCF (block diagram)

page 119

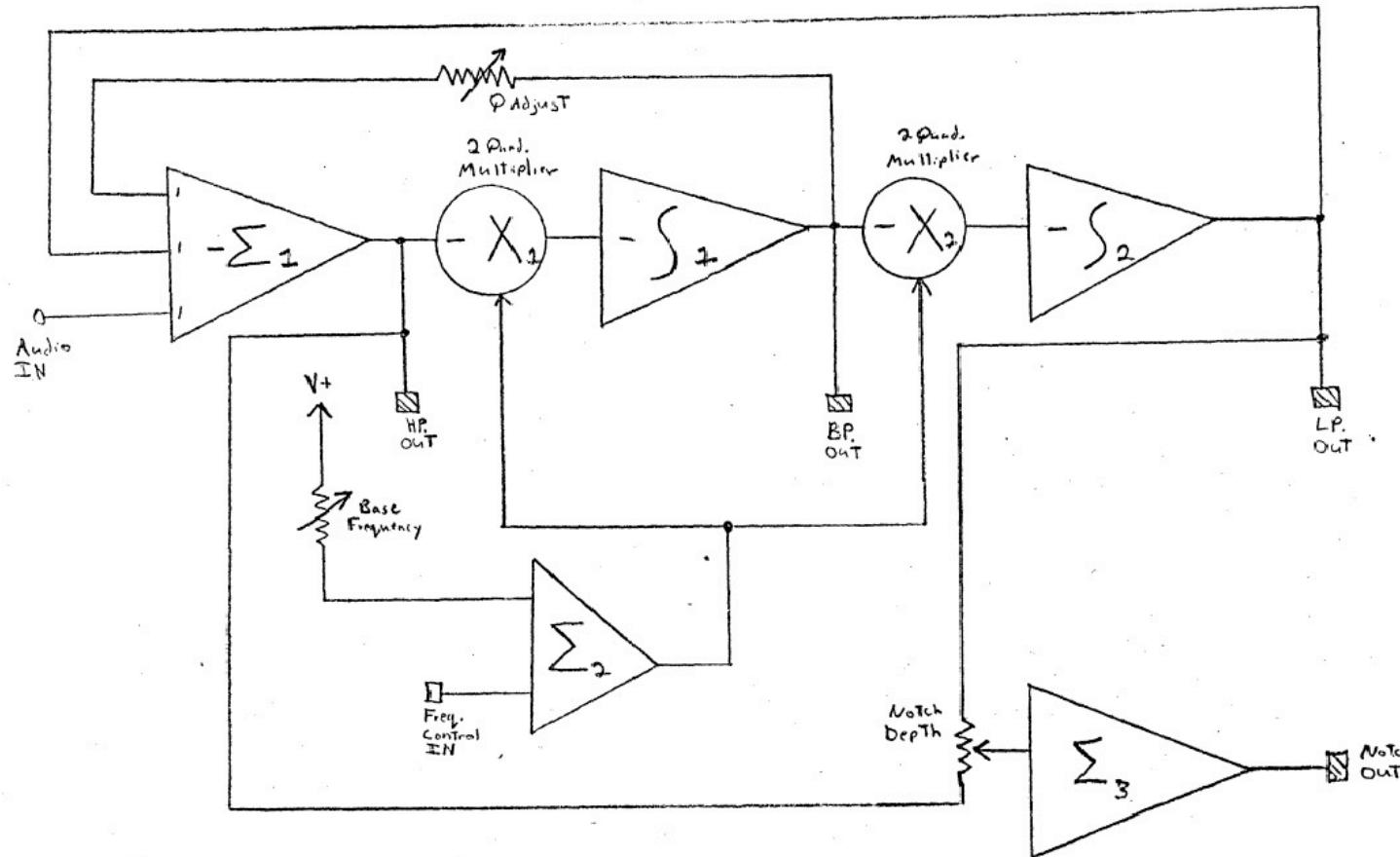


- Analog Computer set up to solve a general Second-Order Differential Equation
 - Exhibits rolloff, damping, and resonance
 - Simultaneous low-pass, bandpass, high-pass, and notch outputs available

Modulars are Analog Computers?

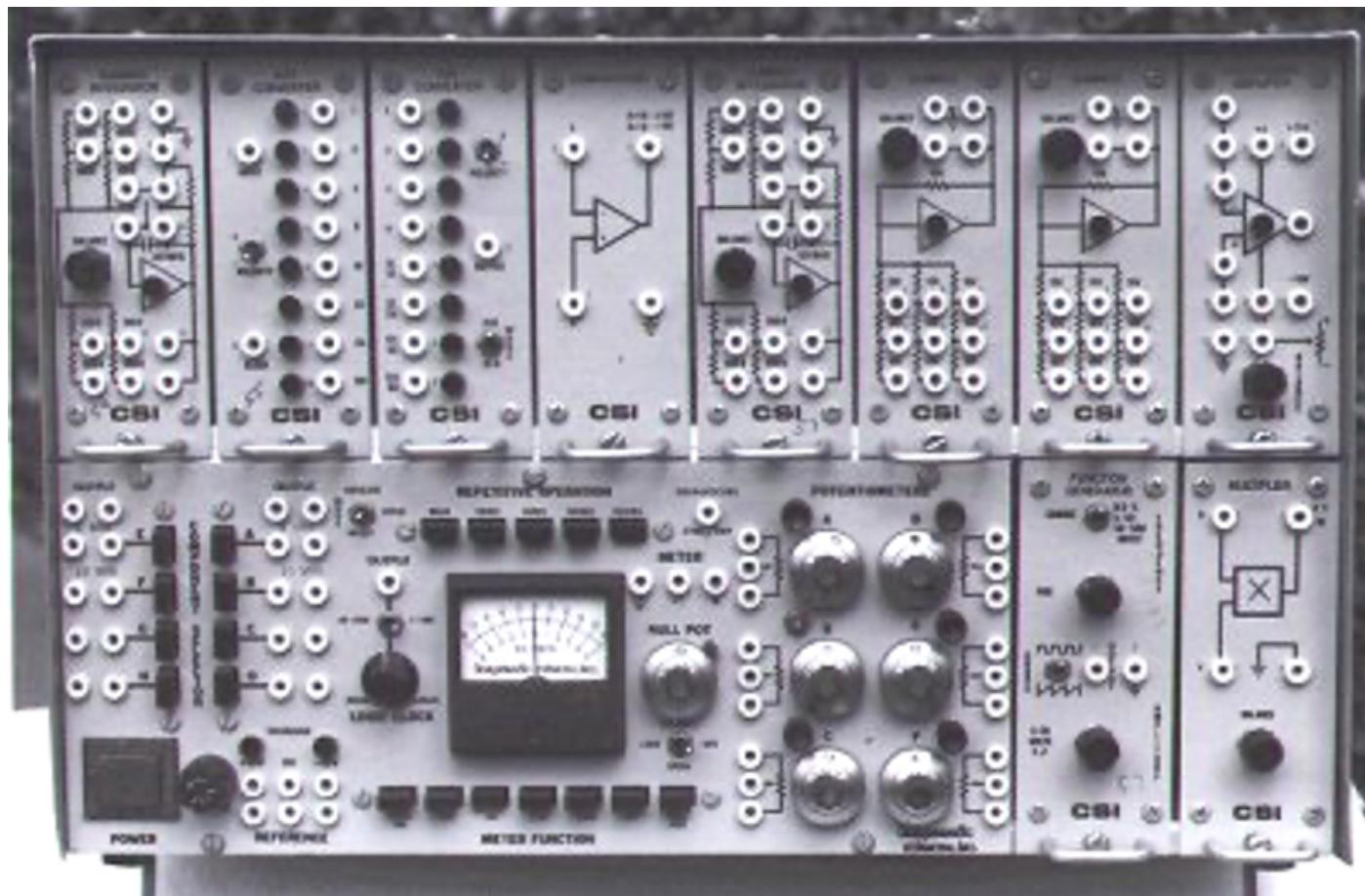


Compumedic Analog Computer from 1971


State Variable Signals

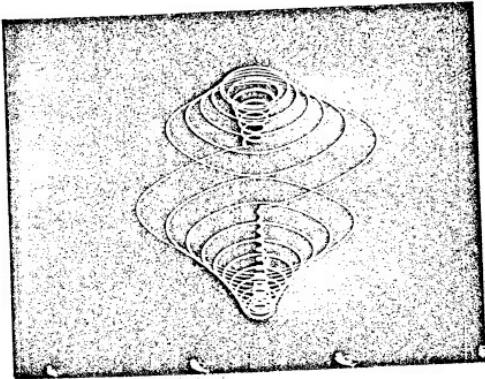

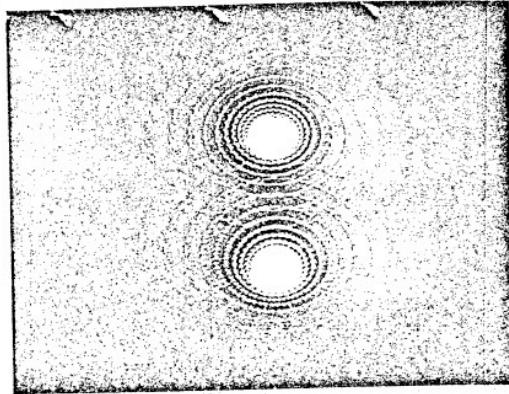
Photo#40 - Crossplot of bandpass vs. lowpass outputs
for a square/sine/triangle mix at the audio
input



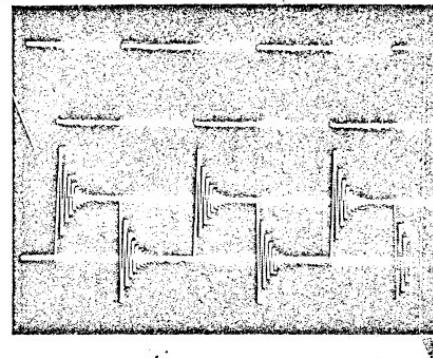
Photo#41 - crossplot of Bandpass vs. Lowpass outputs
for a square wave audio input and a high
frequency pulse added to the control input



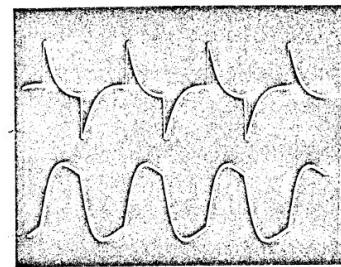Photo#36 - Ring oscillation with resonance



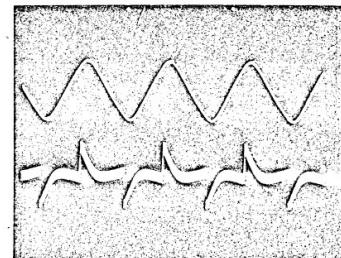High Pass output
Filter waveforms without resonance
(input is still a square wave)
Photo#38



Low Pass
Bandpass
Notch output
Photo#39 - Filter waveforms without resonance
(Square wave input)

Limitations on Filter Performance

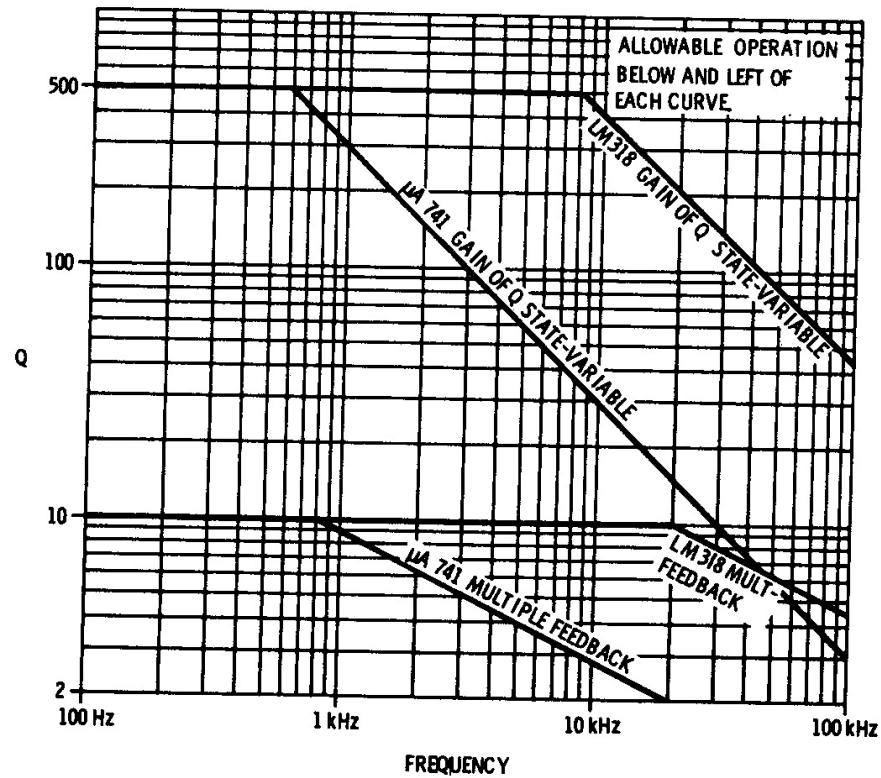


Fig. 7-14. Q and frequency limits for active bandpass filters, small output swings.

- The choice of OpAmp affects how well a given filter will perform
 - Multiple-OpAmp filters can attain higher Q's than single-OpAmp filters
 - Faster OpAmp's work better too
 - Accumulated Phase Shifts can cause oscillation!

Voltage-Controlled Filter


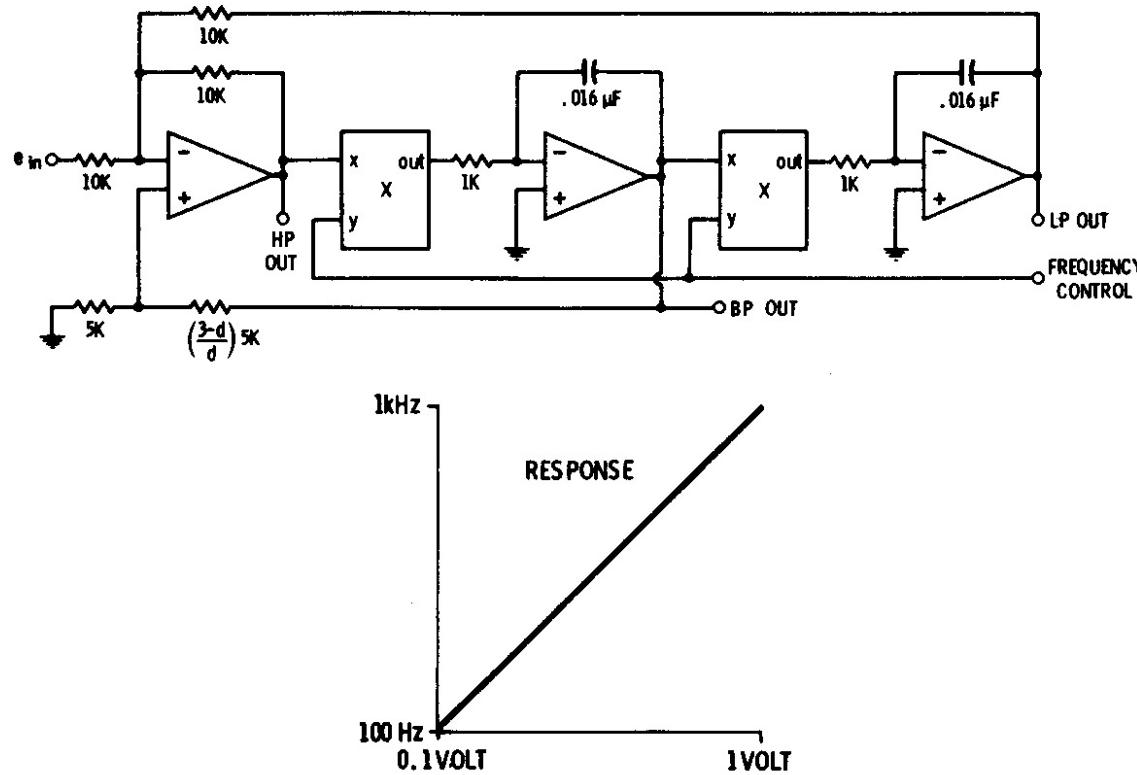


Fig. 9-5. Voltage-controlled filter using IC four-quadrant multipliers.

- Replace integrator input resistors with 2-quadrant multipliers (voltage-controlled amplifiers, or VCA's)
 - Need to tune both VCA's together
 - Results in a wide-range tunable filter!
 - Multiplier can be used to tune Q as well

Switched-Capacitor Tunable Filters

CMOS QUAD BILATERAL SWITCH

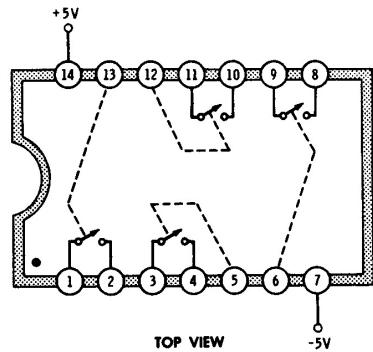

This circuit contains four independent switches that may be used for off-on control of digital or analog signals. Signals to be controlled must be less than +5 and more than -5 volts.


+5 volts applied to pin 13 turns ON the connection between pins 1 and 2. -5 volts applied to pin 13 turns OFF the connection between pins 1 and 2. The other three switches are similarly controlled.

Input impedance to pin 13 is essentially an open circuit. The OFF resistance of pins 1 and 2 is many megohms; the ON resistance is 300 ohms. A lower-impedance, improved version is available as the 4066.

Many types of analog switches are available (e.g., ADG from Analog Devices, etc.)

4016

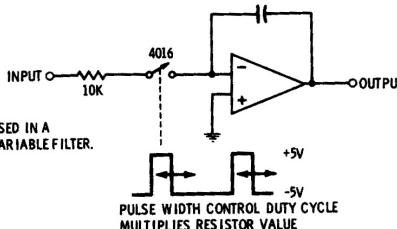(B) Selecting resistors under digital command (D/A conversion).



(C) Duty-cycle modulator provides variable resistance. Switching rate must be much faster than signal frequencies.

Fig. 9-7. Using the 4016 switch.

Filter Cookbook

<https://www.analog.com/media/en/technical-documentation/application-notes/an40f.pdf>

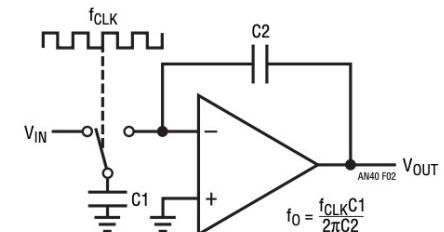


Figure 2. Inverting Switched-Capacitor Integrator

- R is effectively varied proportionally to the On/Off duty cycle
 - Beware of aliasing (max input frequency is under half the switching frequency)
 - Not for High Pass filters (except in feedback configurations)
- Tend to work best for lower-frequencies

Commercial Tunable Filters

CEM 3350


Dual Voltage Controlled State Variable Filter

The CEM 3350 is a dual voltage controlled state-variable filter intended for electronic musical instruments and other signal processing applications. Each filter provides both voltage control of center/cut-off frequency over more than 12 octaves and voltage control of Q from 1/2 to greater than 40. All control scales are exponential, allowing for easier control of the parameters over their wide range. Although the two filters are completely independent, they may be easily interconnected to form a wide variety of filter responses.


Each filter also provides two signal inputs: For signals applied to the fixed gain input, the output will remain constant as the Q is varied, while for signals applied to the variable gain input, the output decreases as Q is increased. The input signal may be proportioned between these two inputs to provide any desired characteristic.

Finally, each filter provides two simultaneous outputs, making directly available low-pass and band-pass, or band-pass and high-pass responses depending upon where the input signal is applied.

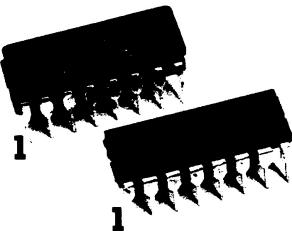Able to operate over a wide supply range, the versatile CEM 3350 allows new and unique filter responses to be created with a high degree of voltage control over the defining parameters.



Block and Connections Diagram

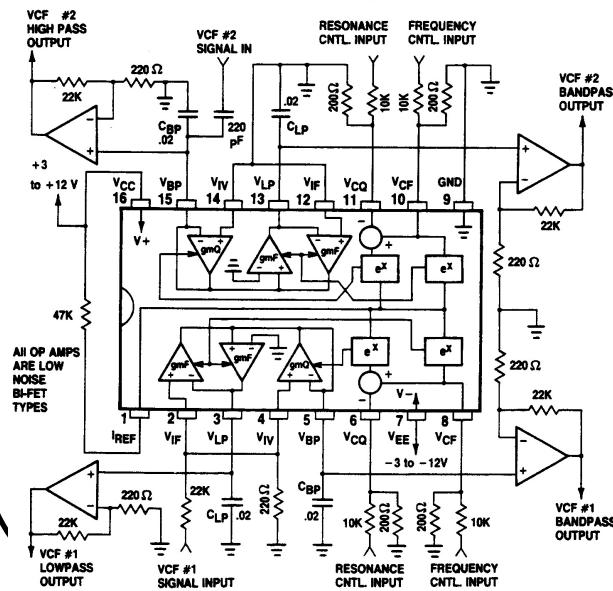

Features:

- Low Cost
- Two Independent State Variable Filters in a Single 16 Pin DIP
- Separate Frequency and Q Control Inputs for Each
- Wide Frequency Sweep and Q Control Range
- Exponential Control Scales for Both Frequency and Q
- Two Simultaneous Outputs on Each: Low-Pass and Band-Pass or Band-Pass and High-Pass Possible
- Two Simultaneous Inputs for Each: Fixed Gain and Variable Gain
- Chip Configurable Into Many Unique V.C. Filters
- Wide Supply Range: $\pm 3V$ to $\pm 16V$

19-1821; Rev 0; 1/100

$$f_C = \frac{f_{CLK}}{100}$$

MAXIM
5th-Order, Lowpass,
Switched-Capacitor Filters

Features

- ◆ 5th-Order, Lowpass Filters
 - Elliptic Response (MAX7418/MAX7421)
 - MAX7422/MAX7425
 - Bessel Response (MAX7419/MAX7423)
 - Butterworth Response (MAX7420/MAX7424)
- ◆ Clock-Turnable Corner Frequency (1Hz to 45kHz)
- ◆ Single-Supply Operation
 - +5V (MAX7418–MAX7421)
 - +3V (MAX7422–MAX7425)
- ◆ Low Power
 - 3mA (Operating Mode)
 - 0.2μA (Shutdown Mode)
- ◆ Available in 8-Pin μMAX Package
- ◆ Low Output Offset: $\pm 4mV$

Ordering Information

PART	TEMP. RANGE	PIN-PACKAGE
MAX7418CUA	0°C to +70°C	8 μMAX
MAX7418EUA	-40°C to +85°C	8 μMAX
MAX7419CUA	0°C to +70°C	8 μMAX
MAX7419EUA	-40°C to +85°C	8 μMAX
MAX7420CUA	0°C to +70°C	8 μMAX
MAX7420EUA	-40°C to +85°C	8 μMAX
MAX7421CUA	0°C to +70°C	8 μMAX
MAX7421EUA	-40°C to +85°C	8 μMAX

Ordering Information continued at end of data sheet.

Applications


ADC Anti-Aliasing CT2 Base Stations
DAC Postfiltering Speech Processing

Selector Guide


PART	FILTER RESPONSE	OPERATING VOLTAGE (V)
MAX7418	r = 1.6	+5
MAX7419	Bessel	+5
MAX7420	Butterworth	+5
MAX7421	r = 1.25	+5

Selector Guide continued at end of data sheet.

Pin Configuration

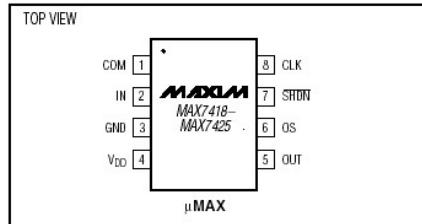


MAXIM

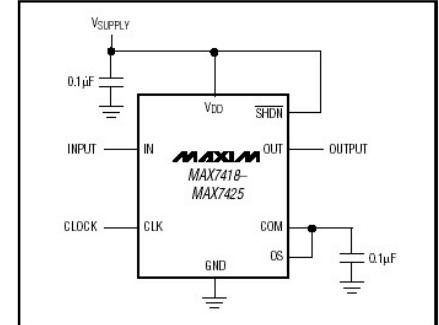

Maxim Integrated Products


Filters from Hong

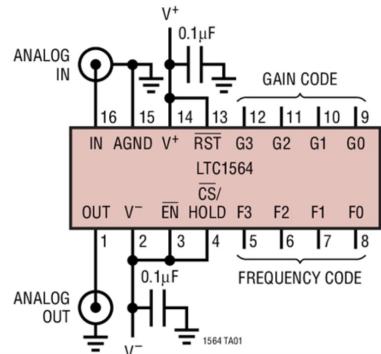Low Noise Programmable Filter with Variable Gain



V⁺ AND V⁻ SUPPLIES CAN BE FROM
1.35V TO 5.25V EACH
TIE F AND G PINS TO V⁺ OR V⁻ TO
SET FREQUENCY AND GAIN
DYNAMIC RANGE 118dB TO 122dB
AT ±5V DEPENDING ON FREQUENCY CODE

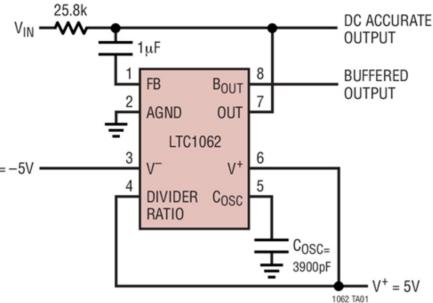10Hz 5th Order Butterworth Lowpass Filter



NOTE: TO ADJUST OSCILLATOR FREQUENCY,
USE A 6800pF CAPACITOR IN SERIES
WITH A 50K POT FROM PIN 5 TO GROUND

LTC1564 Tunable low pass filter 10kHz to 150kHz in steps of 10kHz, 8 pole roll-off, programmable 1-16 gain, 3-10V operation.

LTC1062 parallel 5-pole tunable low pass filter. Absolutely zero DC error because the input and output are connected directly with a wire and the filter damps out the high frequencies.

Note – from 2002!





Biasing

- AC Coupling
- Biasing noninverting input
- Biasing at inverting input


Buffer the voltage divider's output and use it everywhere...

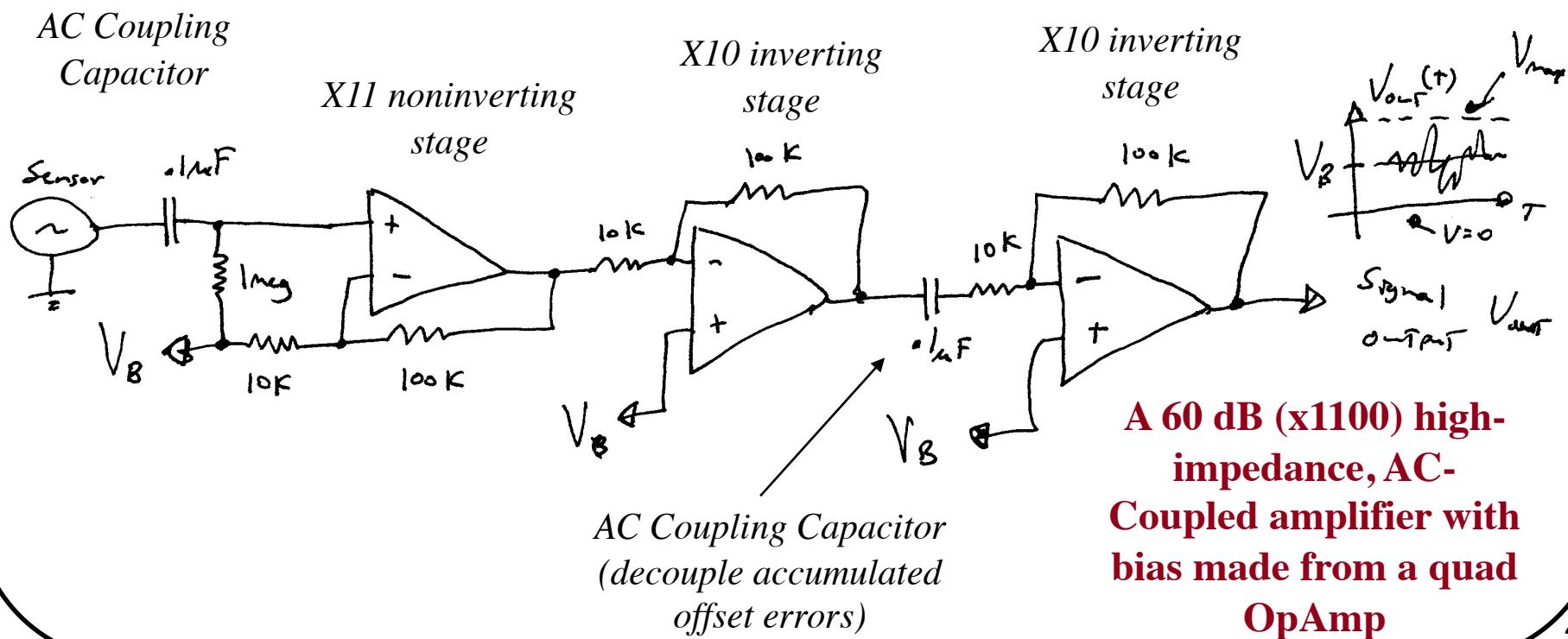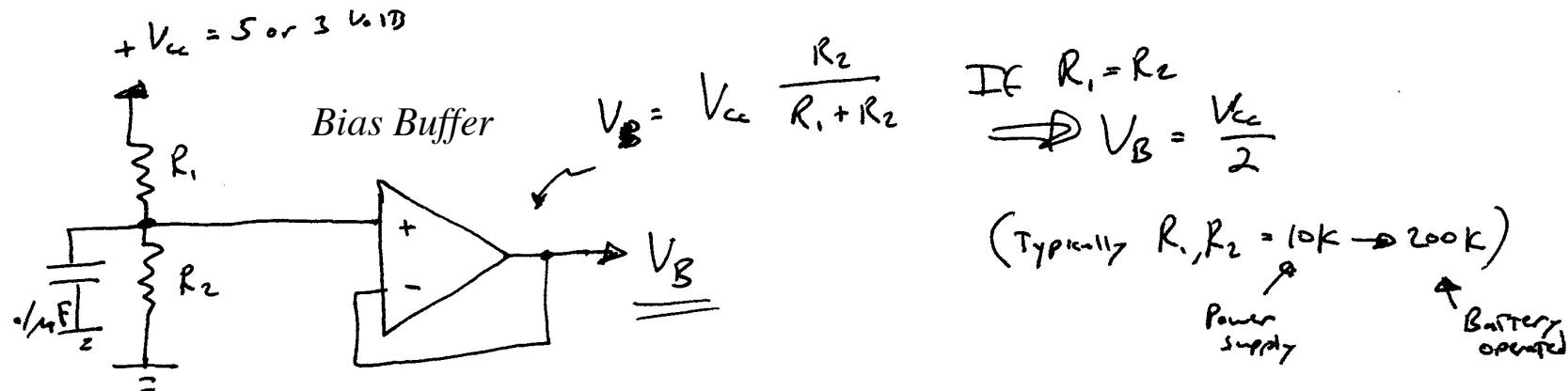Biasing an entire circuit with a Buffered Voltage




Diodes

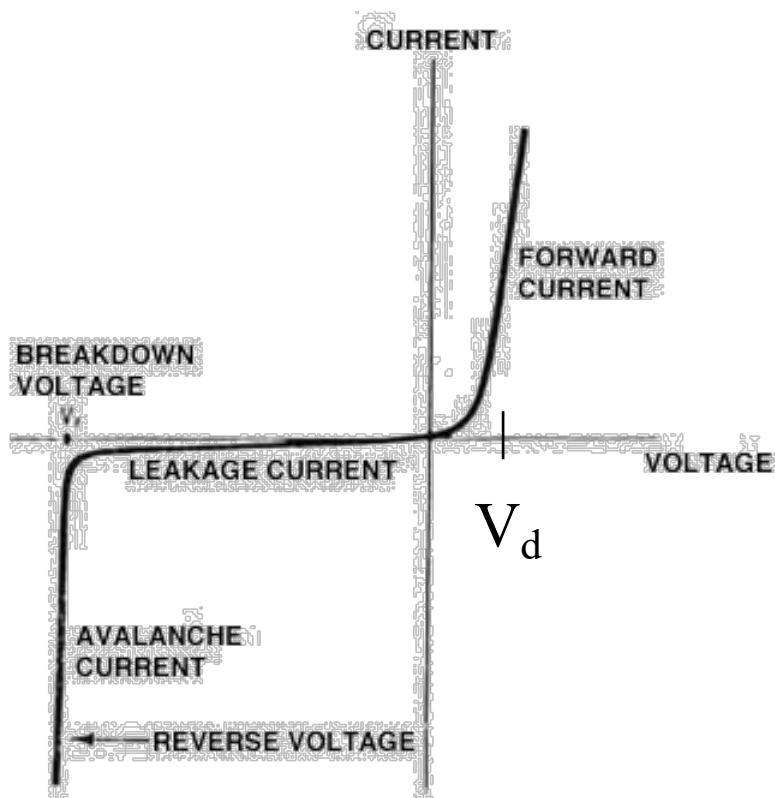- The Diode
 - I/V characteristic, ideal diode, forward drop, zeners





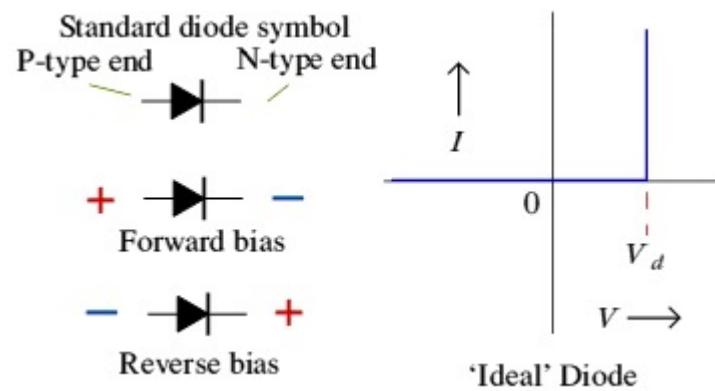
Drops (V_d):
 Si = 0.6 V
 Ge = 0.3 V
 LED = 2.4-3.5 V
 Schottky = .1-.3 V




Basic Diode Circuits

- Limiters/Clampers

 - Passive Limiter - normal and zener

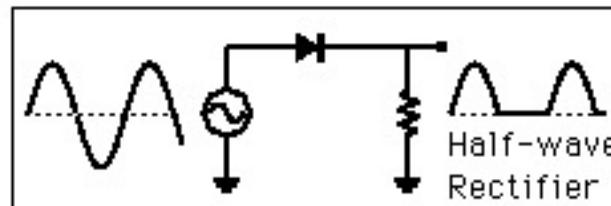
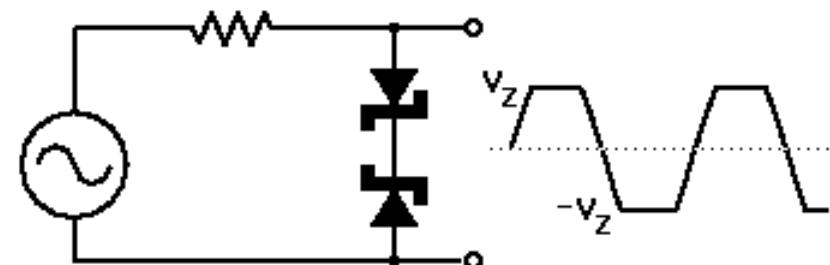
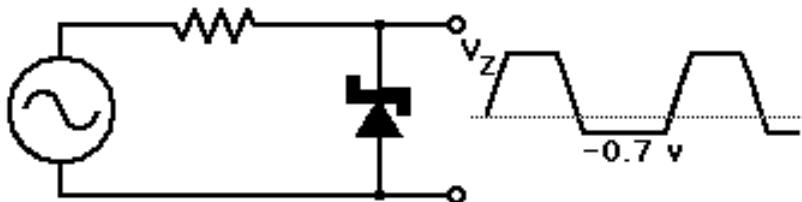


Positive Clammer

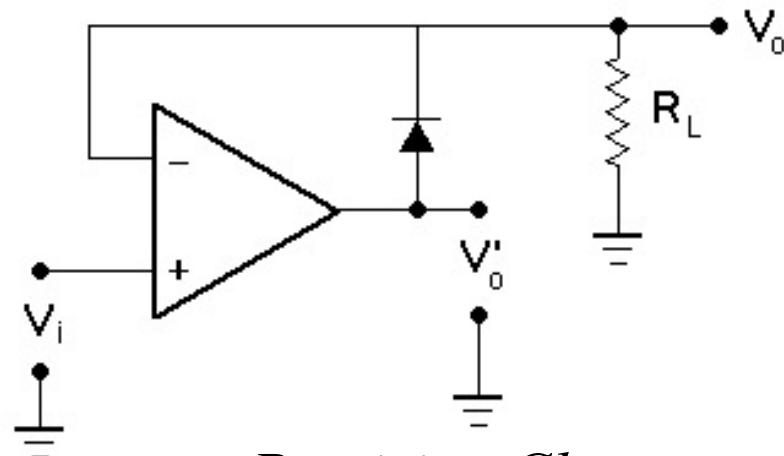


Precision Clammer
(servos out 0.6 V drop)

Bridge Rectifiers → Absolute Value

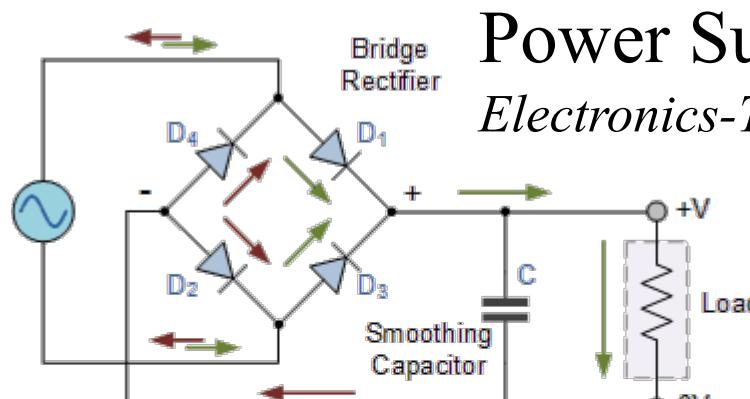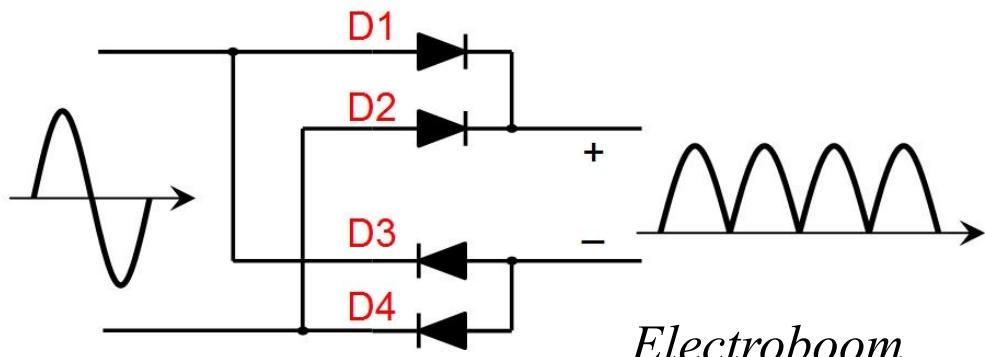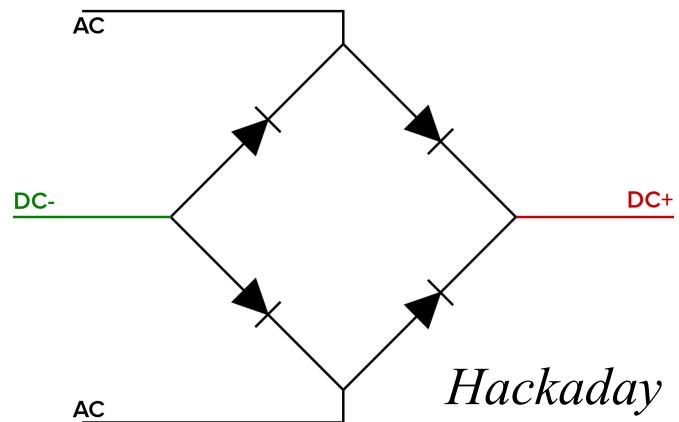



Power Supply
Electronics-Tutorials

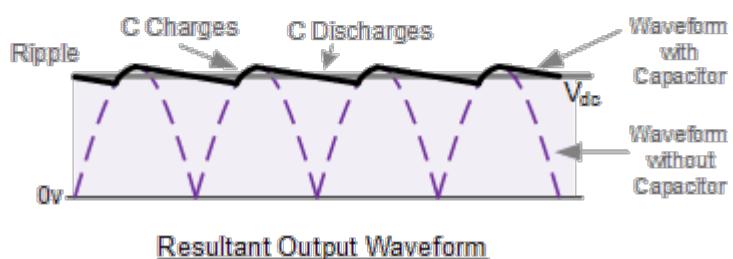

0.6 V diode drop x2!

Voltage Multipliers, etc.

Cascaded Villard doubler

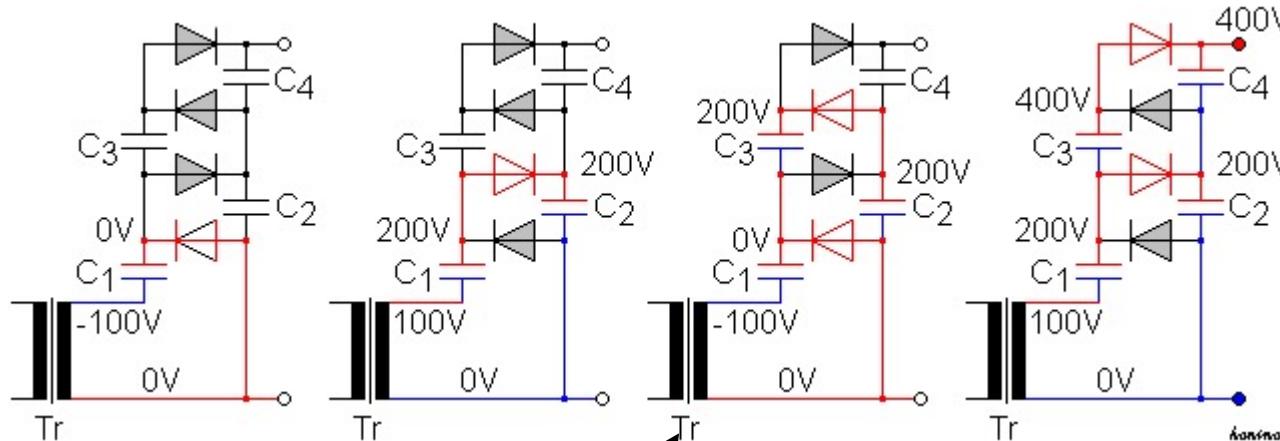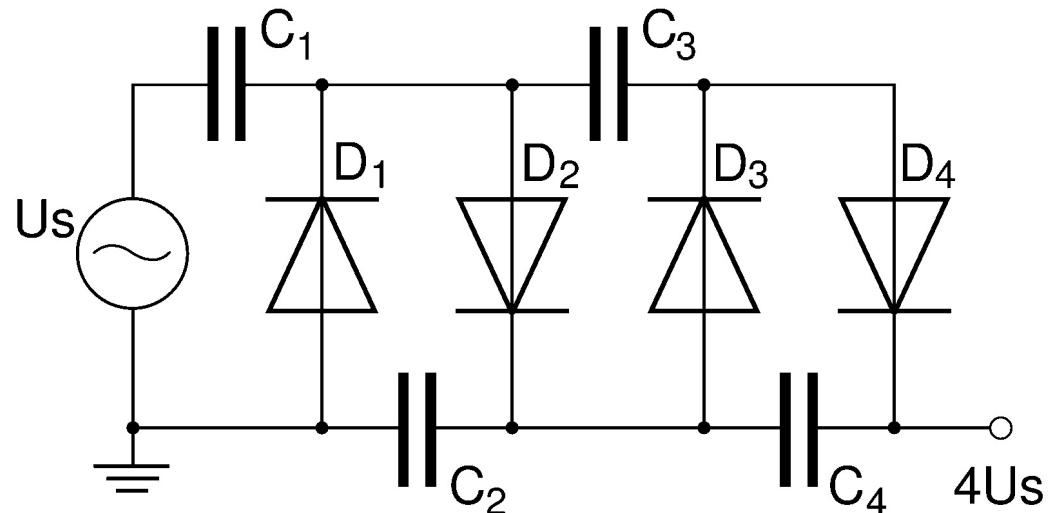


Ref: Wikipedia...



Transformer for isolation

- Diodes don't let capacitors discharge onto source
- AC coupling lets each peak sit atop capacitor voltage
- Each AC peak increments voltage by half-wave height
- Voltage drop at given current increases rapidly (cube) with no. stages, inversely with C, freq

Absolute Value Circuits

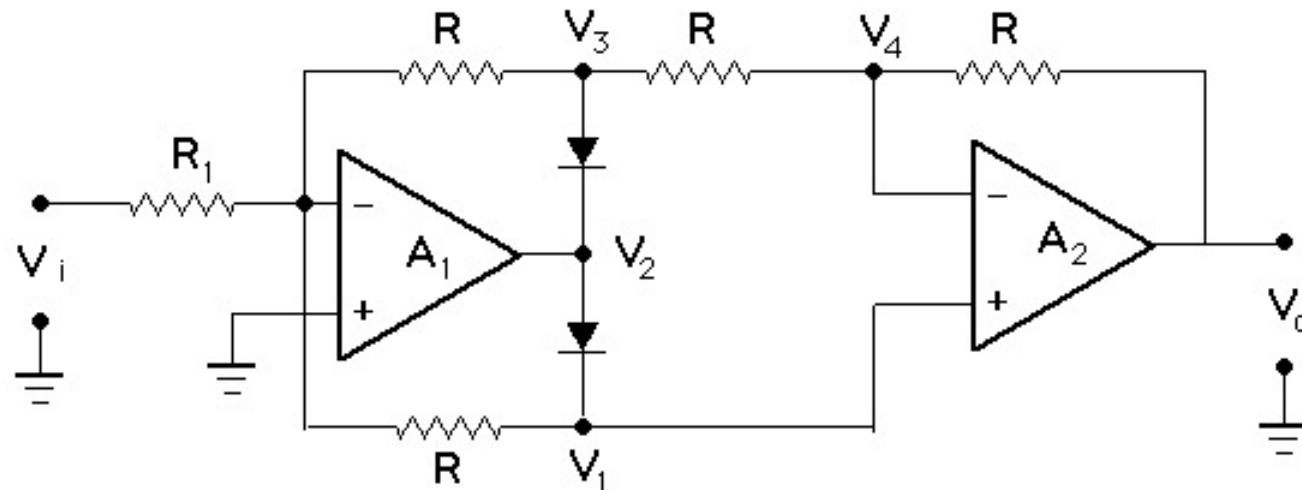


Full Wave Rectifier Circuit

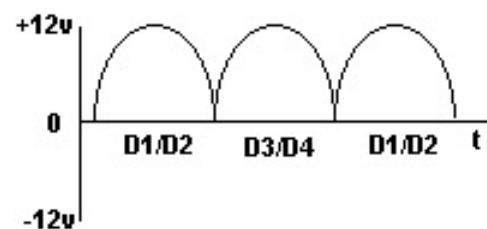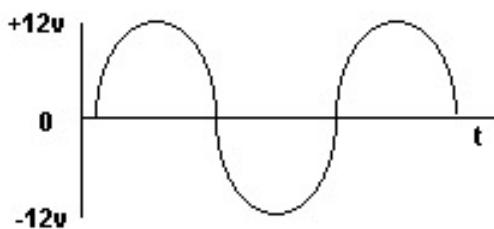

Bottom R is 2/3 top R in A₁?

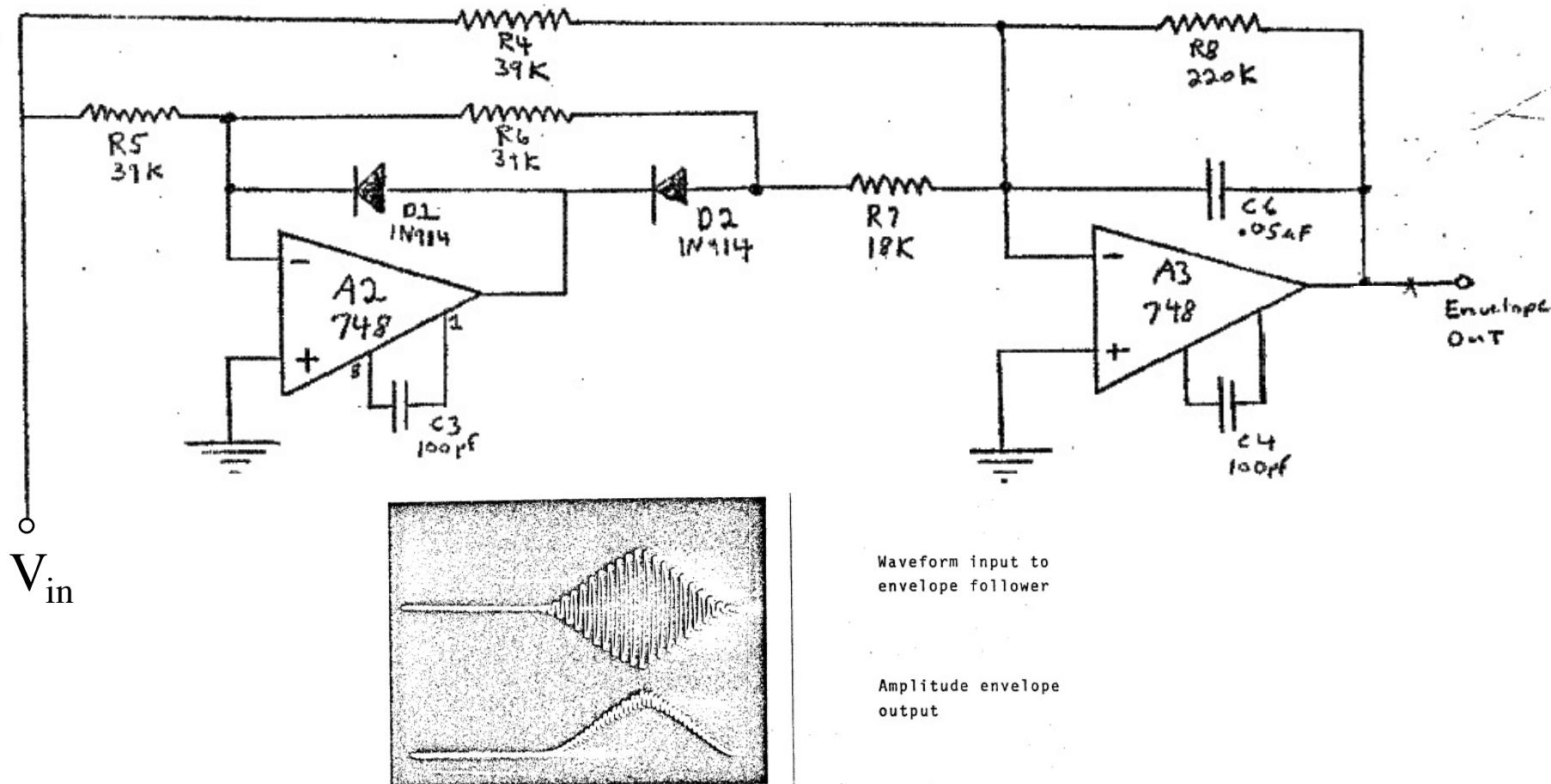Absolute Value Circuit (envelope follower)



- A1 and A2 form an absolute value detector
- C6 integrates the absolute value to give the envelope
- Note that the 748 (and its compensation cap) is long obsolete!

Sampling



- Nyquist: $f_{in} < f_s/2$
- Bandlimited (demodulation) sampling
 - $\Delta f_{in} < f_s/2$
 - Loose absolute phase information
 - Don't know whether phase moves forward or backward
 - Quadrature sampling
 - Bandlimited sampling at t and a quarter-period later



Sampling Aids

- Aliasing for nonperiodic signals??
 - Can miss or miss-sample transients!
 - The Pulse-stretcher to the rescue!
- Sample/Holds
- Analog Multiplexers
- Programmable Gain Amplifiers (PGA's)
- Voltage-Controlled Amplifiers (VCA's)

Peak Detector

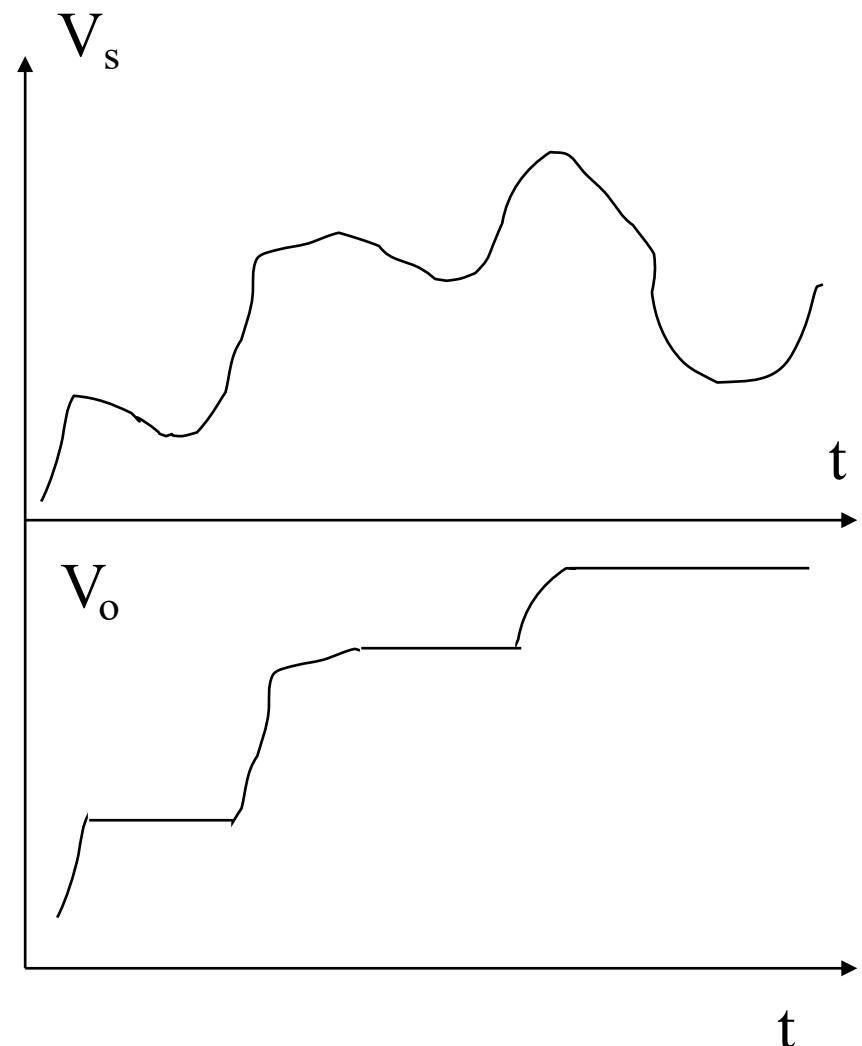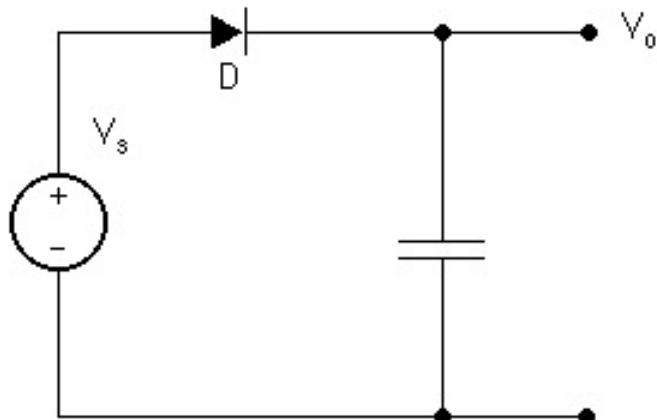

Capacitor holds peaks!

Need reset switch to continue tracking

Peak Detector w. Reset and Gate


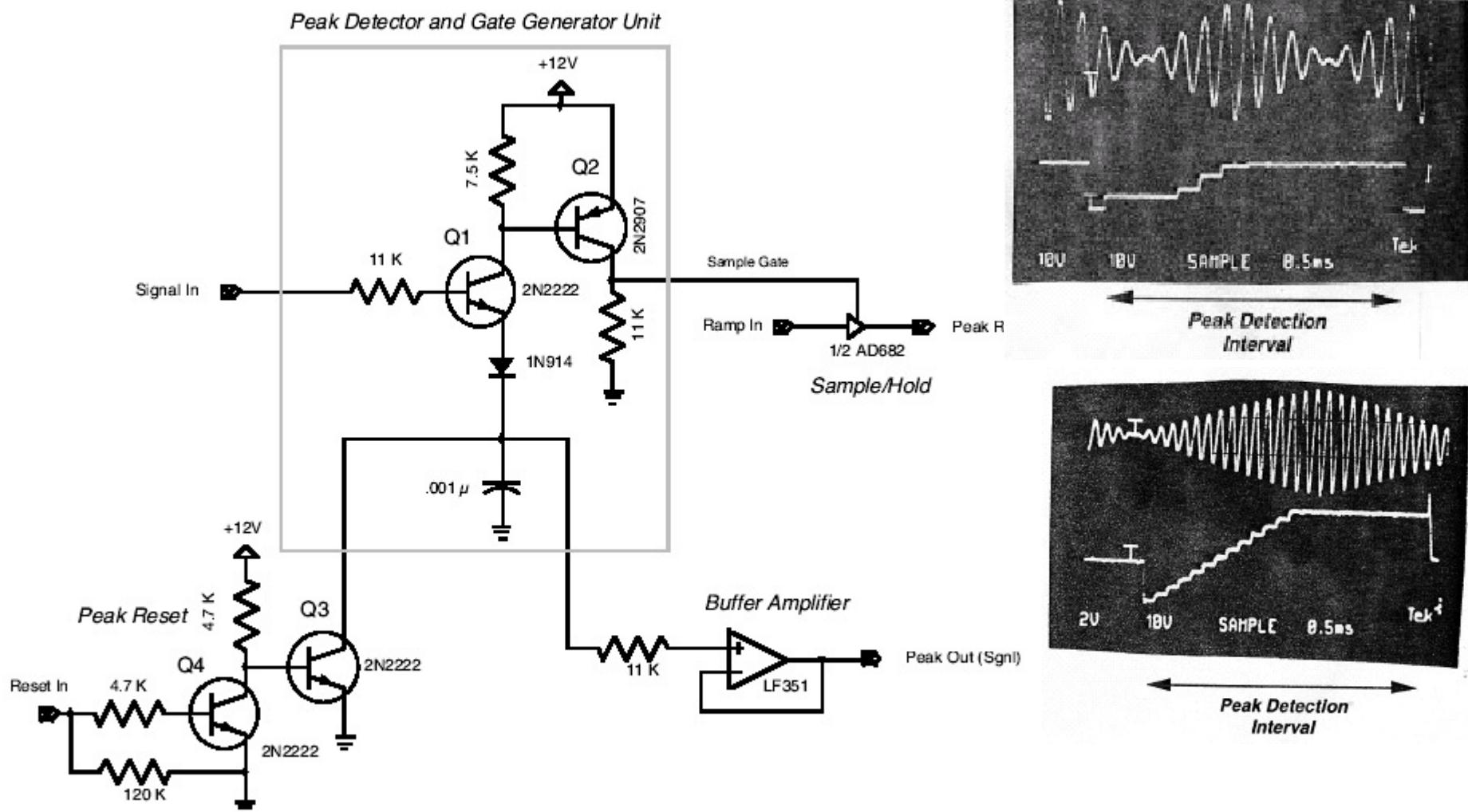



Fig. 4: Peak Sampler Circuit Constructed for Tests

Pulse Stretcher

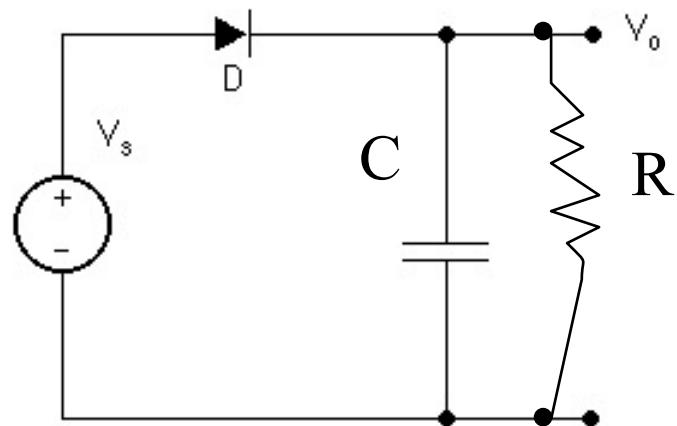


- Resistor continually (and slowly) bleeds capacitor charge
- Automatic “reset”
- Tune time constant to match signal dynamics (so peaks are always followed)

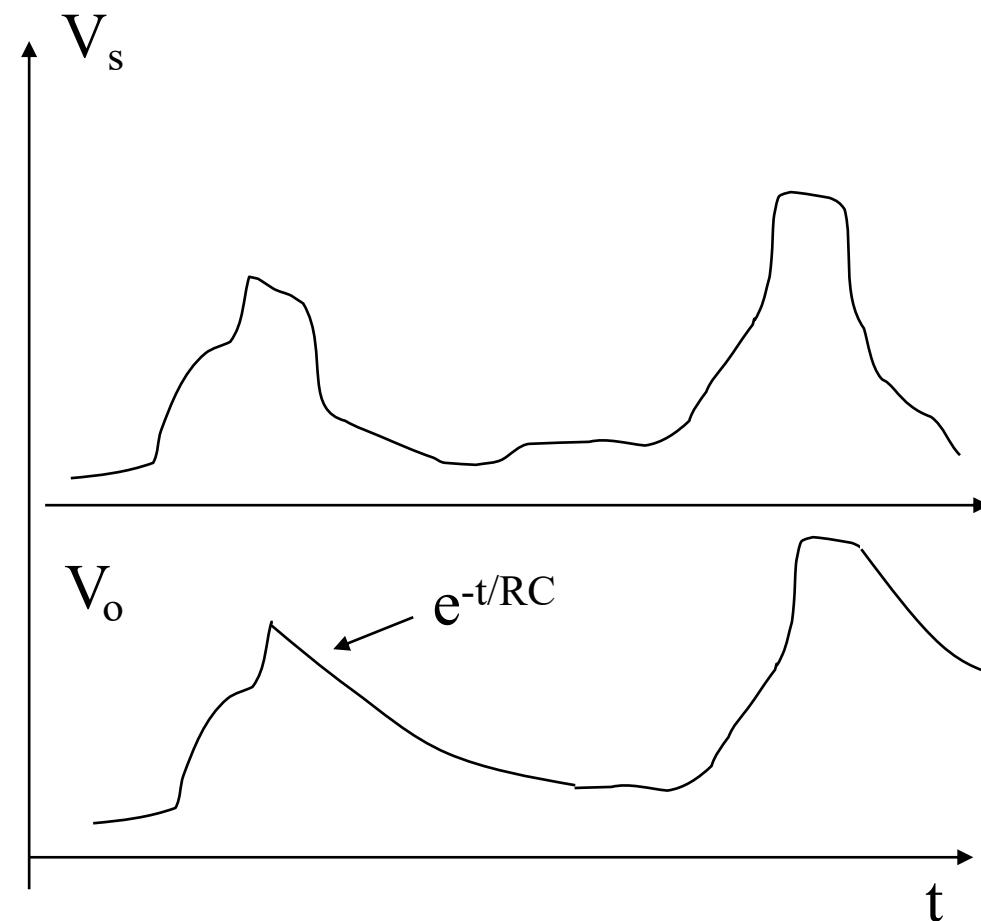
-Enables “lazy” sampling to catch transients



The Basic Sample-Hold Circuit

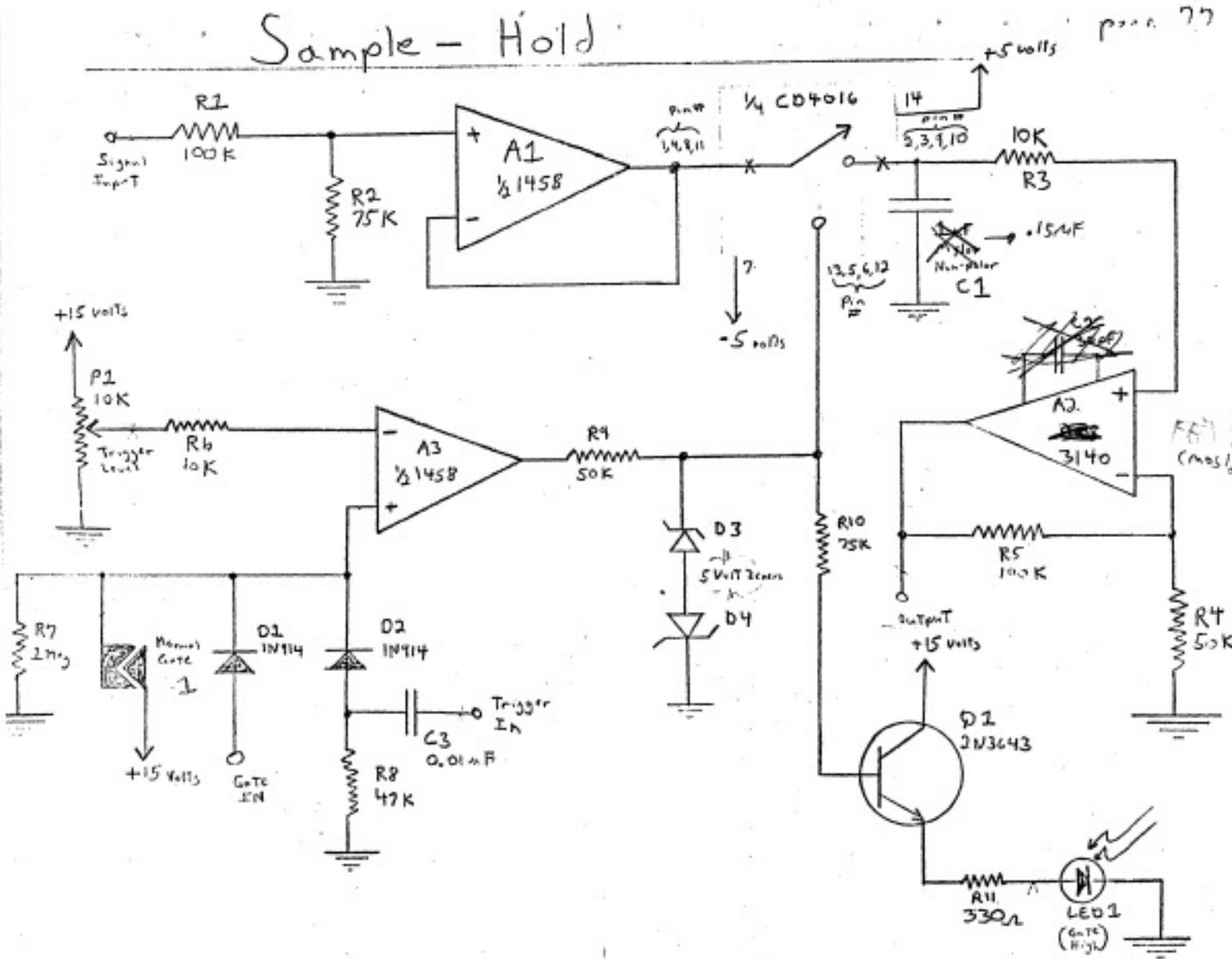


The Sample-Hold (and Track-Hold)

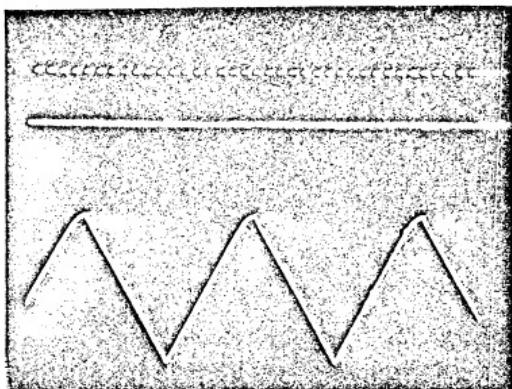


Pulse input to trigger on S/H



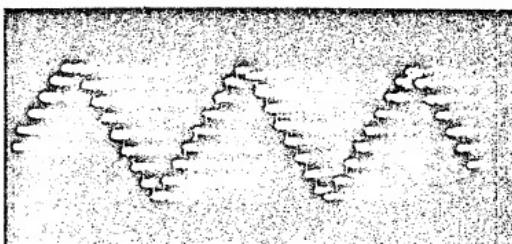Part B:
Square wave applied to the gate input of S/H to yield photo#27



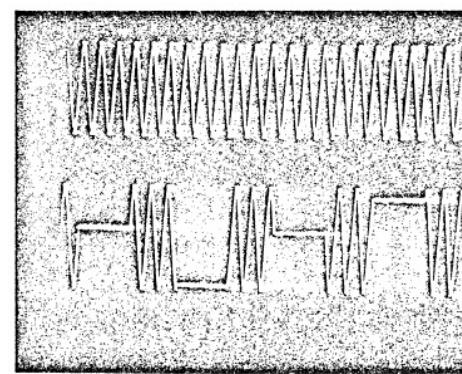Part A:
Output of S/H when waveforms in photo#25 are input



Waveform at S/H's sample input

Output of S/H with above wave at input and the square wave in Part B of Photo#26 at the gate input

- Sample-Hold grabs input signal and holds it upon receipt of a pulse edge
- Track-Hold follows the input signal when the gate is high, but holds (latches) it when the gate is low.
- Sample hold acquires quickly – can use slow ADC.

Sample-Holds


LF198/LF298/LF398, LF198A/LF398A Monolithic Sample-and-Hold Circuits

General Description


The LF198/LF298/LF398 are monolithic sample-and-hold circuits which utilize Bi-FET technology to obtain ultra-high dc accuracy with fast acquisition of signal and low droop rate. Operating as a unity gain follower, dc gain accuracy is 0.002% typical and acquisition time is as low as 6 µs to 0.01%. A bipolar input stage is used to achieve low offset voltage and wide bandwidth. Input offset adjust is accomplished with a single pin, and does not degrade input offset drift. The wide bandwidth allows the LF198 to be included inside the feedback loop of 1 MHz op amps without having stability problems. Input impedance of $10^{10}\Omega$ allows high source impedances to be used without degrading accuracy.

P-channel junction FET's are combined with bipolar devices in the output amplifier to give droop rates as low as 5 mV/min with a 1 µF hold capacitor. The JFET's have much lower noise than MOS devices used in previous designs and do not exhibit high temperature instabilities. The overall design guarantees no feed-through from input to output in the hold mode, even for input signals equal to the supply voltages.


Typical Connection and Performance Curve

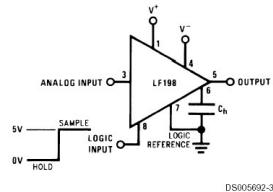

DS005692-32

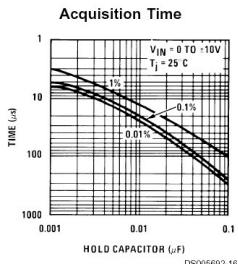

Functional Diagram

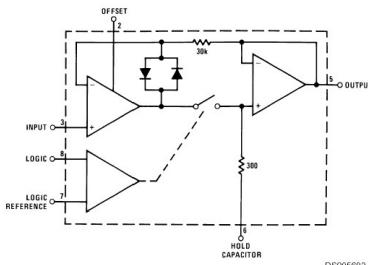

DS005692-1

Simple, 1-channel, ext. cap

19-1469; Rev 0; 7/99

32-Channel Sample/Hold Amplifier with a Single Multiplexed Input

Features

- ◆ 32-Channel Sample/Hold
- ◆ Output Clamping
- ◆ 0.01% Accuracy of Acquired Signal
- ◆ 0.01% Linearity Error
- ◆ Fast Acquisition Time: 2.5µs
- ◆ Low Droop Rate: 1mV/sec
- ◆ Low Hold Step: 0.25mV
- ◆ Wide Output Voltage Range: +7V to -4V


Ordering Information

PART	TEMP. RANGE	PIN-PACKAGE	ROUT (Ω)
MAX5165LCCM	0°C to +70°C	48 TQFP	50
MAX5165MCCM	0°C to +70°C	48 TQFP	500
MAX5165NCCM	0°C to +70°C	48 TQFP	1k
MAX5165LECM	-40°C to +85°C	48 TQFP	50
MAX5165MECM	-40°C to +85°C	48 TQFP	500
MAX5165NECM	-40°C to +85°C	48 TQFP	1k

Applications

- Automatic Test Equipment (ATE)
Industrial Process Controls
Arbitrary Function Generators
Avionics Equipment

Pin Configuration

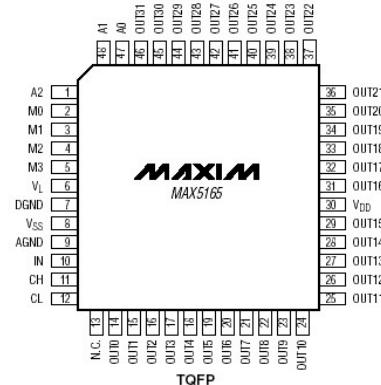

Multiple S/H on one input for fast acquisition

Analog Multiplexers

CD4051BM/CD4051BC Single 8-Channel Analog Multiplexer/Demultiplexer

CD4052BM/CD4052BC Dual 4-Channel Analog Multiplexer/Demultiplexer

CD4053BM/CD4053BC Triple 2-Channel Analog Multiplexer/Demultiplexer

General Description

These analog multiplexers/demultiplexers are digitally controlled analog switches having low "ON" impedance and very low "OFF" leakage currents. Control of analog signals up to $15V_{pp}$ can be achieved by digital signal amplitudes of 3–15V. For example, if $V_{DD} = 5V$, $V_{SS} = 0V$ and $V_{EE} = -5V$, analog signals from $-5V$ to $+5V$ can be controlled by digital inputs of 0–5V. The multiplexer circuits dissipate extremely low quiescent power over the full $V_{DD} – V_{SS}$ and $V_{DD} – V_{EE}$ supply voltage ranges, independent of the logic state of the control signals. When a logical "1" is present at the inhibit input terminal all channels are "OFF".

CD4051BM/CD4051BC is a single 8-channel multiplexer having three binary control inputs, A, B, and C, and an inhibit input. The three binary signals select 1 of 8 channels to be turned "ON" and connect the input to the output.

CD4052BM/CD4052BC is a differential 4-channel multiplexer having two binary control inputs, A and B, and an inhibit input. The two binary input signals select 1 or 4 pairs of channels to be turned on and connect the differential analog inputs to the differential outputs.




CD4053BM/CD4053BC is a triple 2-channel multiplexer having three separate digital control inputs, A, B, and C, and

an inhibit input. Each control input selects one of a pair of channels which are connected in a single-pole double-throw configuration.

Features

- Wide range of digital and analog signal levels: digital 3–15V, analog to $15V_{pp}$
- Low "ON" resistance: 80Ω (typ.) over entire $15V_{pp}$ signal-input range for $V_{DD} – V_{EE} = 15V$
- High "OFF" resistance: channel leakage of $\pm 10\text{ pA}$ (typ.) at $V_{DD} – V_{EE} = 10V$
- Logic level conversion for digital addressing signals of 3–15V ($V_{DD} – V_{SS} = 3–15V$) to switch analog signals to $15V_{pp}$ ($V_{DD} – V_{EE} = 15V$)
- Matched switch characteristics: $\Delta R_{ON} = 5\Omega$ (typ.) for $V_{DD} – V_{EE} = 15V$
- Very low quiescent power dissipation under all digital-control input and supply conditions: $1\text{ }\mu\text{W}$ (typ.) at $V_{DD} – V_{SS} = V_{DD} – V_{EE} = 10V$
- Binary address decoding on chip

Connection Diagrams

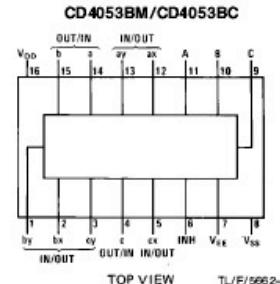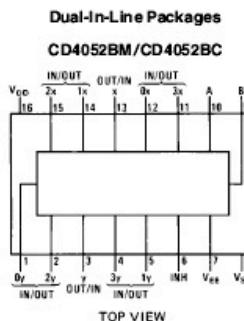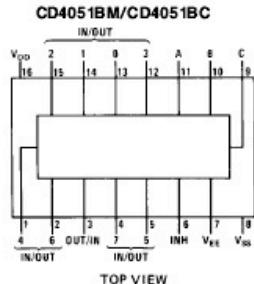

Order Number CD4051B, CD4052B, or CD4053B



CMOS

4-/8-Channel Analog Multiplexers

AD7501/AD7502/AD7503

FEATURES

DTL/TTL/CMOS Direct Interface


Power Dissipation: $30\text{ }\mu\text{W}$

$R_{ON} = 170\ \Omega$


Standard 16-Lead DIPs and 20-Terminal Surface Mount Packages

FUNCTIONAL BLOCK DIAGRAM

AD7501/AD7503

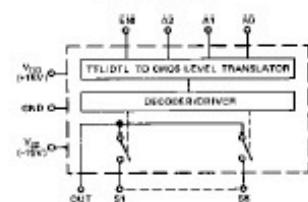

AD7502

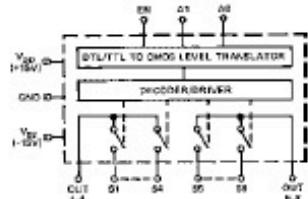

AD7503


A ₂	A ₁	A ₀	EN	"ON"
0	0	0	1	1
0	0	1	1	2
0	1	0	1	3
0	1	1	1	4
1	0	0	1	5
1	0	1	1	6
1	1	0	1	7
1	1	1	1	8
X	X	X	0	None

A ₂	A ₁	A ₀	EN	"ON"
0	0	0	0	1
0	0	1	0	2
0	1	0	0	3
0	1	1	0	4
1	0	0	0	5
1	0	1	0	6
1	1	0	0	7
1	1	1	0	8
X	X	X	1	None

AD7502

A ₂	A ₁	EN	"ON"
0	0	0	1 & 5
0	1	0	2 & 6
1	0	0	3 & 7
1	1	0	4 & 8
X	X	0	None

Programmable Gain Amplifiers

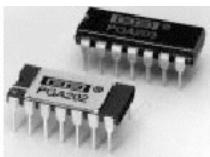

PGA202/203

PGA206
PGA207

Digitally Controlled Programmable-Gain INSTRUMENTATION AMPLIFIER

FEATURES


- DIGITALLY PROGRAMMABLE GAINS:
DECADE MODEL—PGA202
GAINS OF 1, 10, 100, 1000
BINARY MODEL—PGA203
GAINS OF 1, 2, 4, 8
- LOW BIAS CURRENT: 50pA max
- FAST SETTLING: 2 μ s to 0.01%
- LOW NON-LINEARITY: 0.012% max
- HIGH CMRR: 80dB min
- NEW TRANSCONDUCTANCE CIRCUITRY
- LOW COST

APPLICATIONS

- DATA ACQUISITION SYSTEMS
- AUTO-RANGING CIRCUITS
- DYNAMIC RANGE EXPANSION
- REMOTE INSTRUMENTATION
- TEST EQUIPMENT

DESCRIPTION

The PGA202 is a monolithic instrumentation amplifier with digitally controlled gains of 1, 10, 100, and 1000. The PGA203 provides gains of 1, 2, 4, and 8. Both have TTL or CMOS-compatible inputs for easy microprocessor interface. Both have FET inputs and a new transconductance circuitry that keeps the bandwidth nearly constant with gain. Gain and offsets are laser trimmed to allow use without any external components. Both amplifiers are available in ceramic or plastic packages. The ceramic package is specified over the full industrial temperature range while the plastic package covers the commercial range.

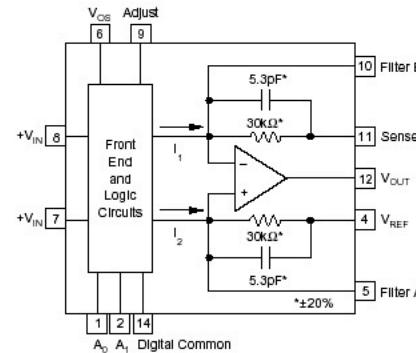

High-Speed Programmable Gain INSTRUMENTATION AMPLIFIER

FEATURES

- DIGITALLY PROGRAMMABLE GAINS:
PGA206: G=1, 2, 4, 8/V
PGA207: G=1, 2, 5, 10/V
- TRUE INSTRUMENTATION AMP INPUT
- FAST SETTLING: 3.5 μ s to 0.01%
- FET INPUT: I_B = 100pA max
- INPUT PROTECTION: ±40V
- LOW OFFSET VOLTAGE: 1.5mV max
- 16-PIN DIP, SOL-16 SOIC PACKAGES

APPLICATIONS

- MULTIPLE-CHANNEL DATA ACQUISITION
- MEDICAL, PHYSIOLOGICAL AMPLIFIER
- PC-CONTROLLED ANALOG INPUT BOARDS


DESCRIPTION

The PGA206 and PGA207 are digitally programmable gain instrumentation amplifiers that are ideally suited for data acquisition systems.

The PGA206 and PGA207's fast settling time allows multiplexed input channels for excellent system efficiency. FET inputs eliminate I_B errors due to analog multiplexer series resistance.


Gains are selected by two CMOS/TTL-compatible address lines. Analog inputs are internally protected for overloads up to ±40V, even with the power supplies off. The PGA206 and PGA207 are laser-trimmed for low offset voltage and low drift.

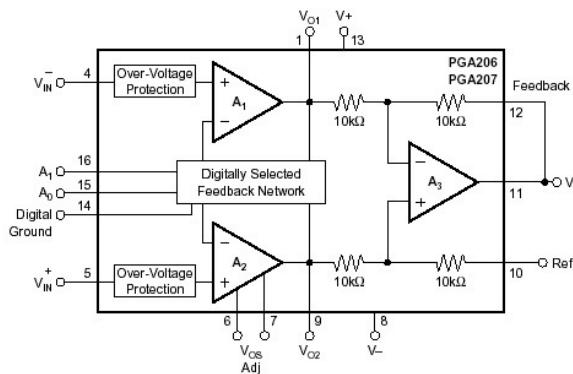The PGA206 and PGA207 are available in 16-pin plastic DIP and SOL-16 surface-mount packages. Both are specified for -40°C to +85°C operation.



Front end of the OTA
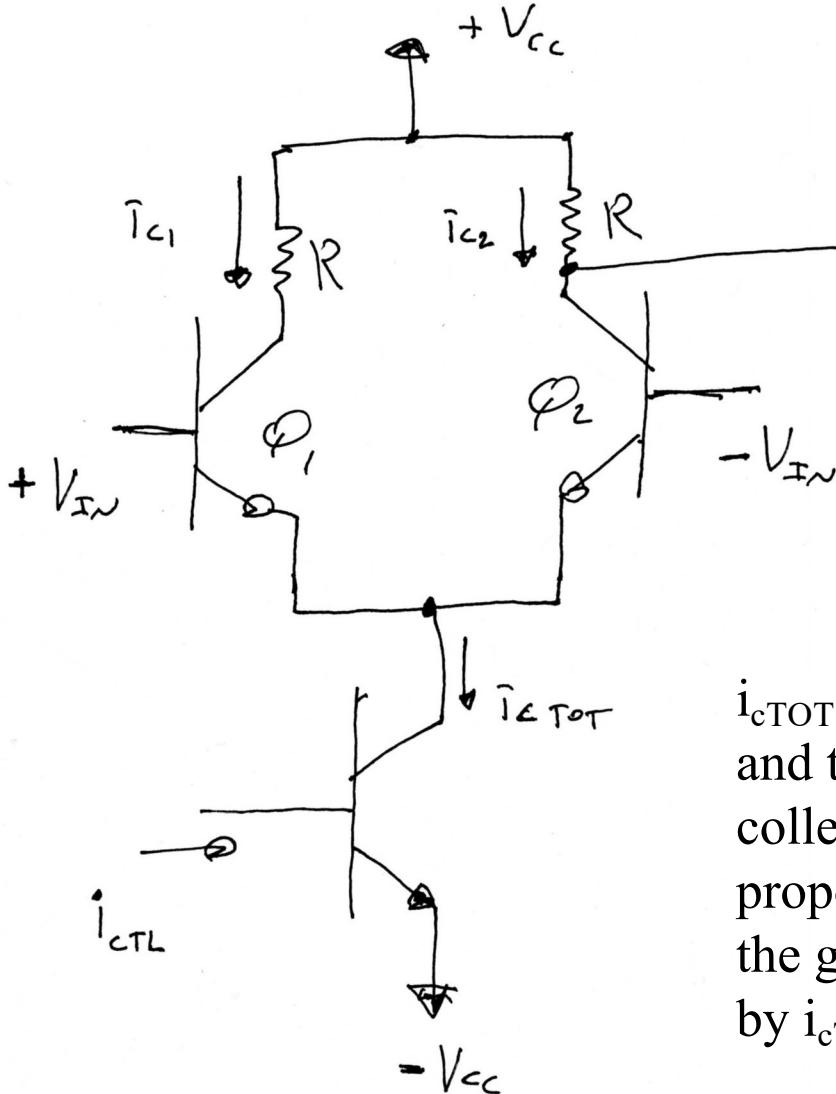
$$I_{c\text{tot}} = i_{c1} + i_{c2} = \beta i_{\text{CTL}}$$




OTAs have
current outputs

Buffer

Other
Stages

i_{out}

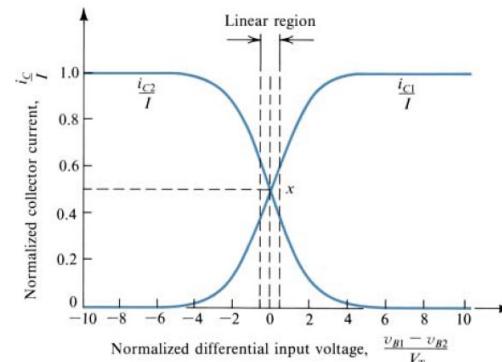


MTU ECE Diff Amp Notes


Increasing $+V_{IN}$ increases i_{c1} ,
which decreases i_{c2} (for fixed $-V_{IN}$)
since the sum of i_{c1} and i_{c2} must
equal $i_{c\text{TOT}}$

$i_{c\text{TOT}}$ is proportional to i_{CTL} ,
and the voltage across the
collector resistors is
proportional to $i_{c\text{TOT}}$, hence
the gain of this circuit is set
by $i_{c\text{TOT}}$

LM13700 Datasheet

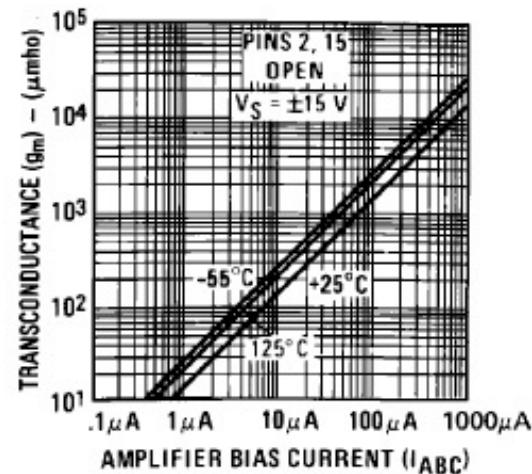

Voltage Controlled Amplifiers

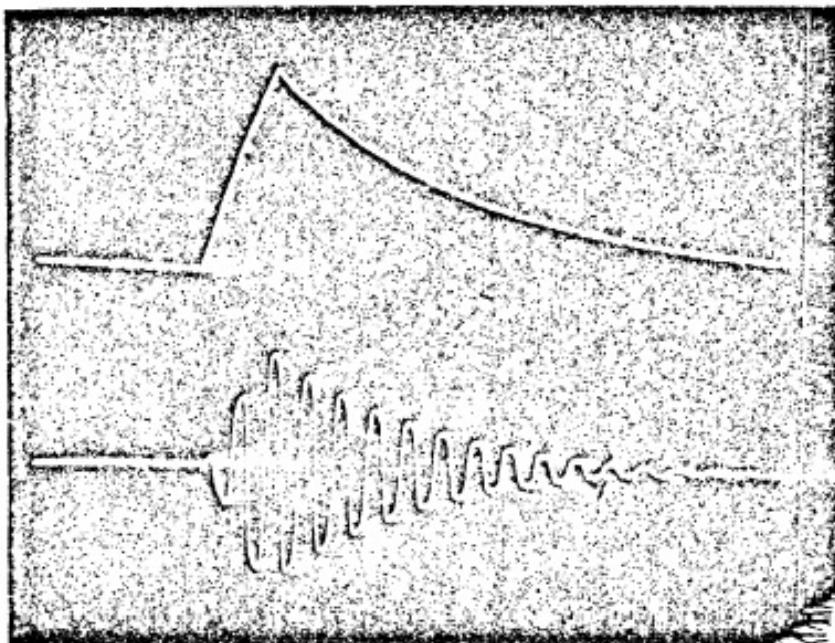

Control voltage input
to VCA

Output of VCA

VCA output for sinusoidal input and given control voltage

$$V_{\text{out}} = V_{\text{in}} * V_{\text{ctl}} \text{ (or } 0 \text{ if } V_{\text{ctl}} < 0)$$

Voltage-Controlled Amplifiers (VCA)

BB | Burr-Brown Products
from Texas Instruments

www.ti.com

WIDEBAND VOLTAGE CONTROLLED AMPLIFIER

FEATURES

- WIDE GAIN CONTROL RANGE: 77dB
- SMALL PACKAGE: SO-8
- WIDE SIGNAL BANDWIDTH: 30MHz
- LOW VOLTAGE NOISE: $2.2\text{nV}/\sqrt{\text{Hz}}$
- FAST GAIN SLEW RATE: $300\text{dB}/\mu\text{s}$

DESCRIPTION

The VCA610 is a wideband, continuously variable, voltage-controlled gain amplifier. It provides linear-dB gain control with high impedance inputs. It is designed to be used as a flexible gain-control element in a variety of electronic systems.

The VCA610 has a gain-control range of 77dB (-38.5dB to $+38.5\text{dB}$) providing both gain and attenuation for maximum flexibility in a small SO-8. The broad attenuation range can be used for gradual or controlled channel turn-on and turn-off for applications in which abrupt gain changes can create artifacts or other errors. In addition, the output can be disabled to provide -77dB of attenuation. Group delay variation with gain is typically less than $\pm 2\text{ns}$ across a bandwidth of 1MHz to 15MHz.

The VCA610 has a noise figure of 3.5dB (with an R_s of 200Ω) including the effects of both current and voltage noise. Instantaneous output dynamic range is 70dB for gains of 0dB to $+38.5\text{dB}$ with 1MHz noise bandwidth. The output is capable of driving 100Ω . The high-speed, $300\text{dB}/\mu\text{s}$, gain-control signal is a unipolar (0V to -2V) voltage that varies the gain linearly in dB/V over a -38.5dB to $+38.5\text{dB}$ range.




VCA610

APPLICATIONS

- OPTICAL DISTANCE MEASUREMENT
- AGC AMPLIFIERS
- ULTRASOUND
- SONAR
- ACTIVE FILTERS
- LOG AMPLIFIERS
- IF CIRCUITS
- CCD CAMERAS

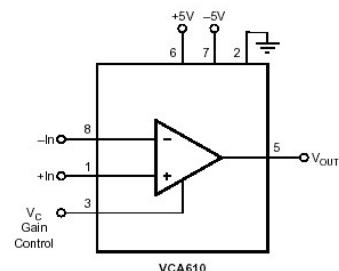The VCA610 is designed with a very fast overload recovery time of only 200ns. This allows a large signal transient to overload the output at high gain, without obscuring low-level signals following closely behind. The excellent overload recovery time and distortion specifications optimize this device for low-level doppler measurements.



**TEXAS
INSTRUMENTS**

**ANALOG
DEVICES**

Also AD603

AD600/AD602*

FEATURES

Two Channels with Independent Gain Control

"Linear in dB" Gain Response

Two Gain Ranges:

AD600: 0 dB to 40 dB

AD602: -10 dB to +30 dB

Accurate Absolute Gain: ± 0.3 dB

Low Input Noise: $1.4 \text{nV}/\sqrt{\text{Hz}}$

Low Distortion: -60dBc THD at $\pm 1 \text{V}$ Output

High Bandwidth: DC to 35 MHz (-3 dB)

Stable Group Delay: $\pm 2 \text{ ns}$

Low Power: 125 mW (Max) per Amplifier

Signal Gating Function for Each Amplifier

Drives High-Speed A/D Converters

MIL-STD-883-Compliant and DESC Versions Available

APPLICATIONS

Ultrasound and Sonar Time-Gain Control

High-Performance Audio and RF AGC Systems

Signal Measurement

PRODUCT DESCRIPTION


The AD600 and AD602 dual channel, low noise variable gain amplifiers are optimized for use in ultrasound imaging systems, but are applicable to any application requiring very precise gain, low noise and distortion, and wide bandwidth. Each independent channel provides a gain of 0 dB to $+40$ dB in the AD600 and -10 dB to $+30$ dB in the AD602. The lower gain of the AD602 results in an improved signal-to-noise ratio at the output. However, both products have the same $1.4 \text{nV}/\sqrt{\text{Hz}}$ input noise spectral density. The decibel gain is directly proportional to the control voltage, is accurately calibrated, and is supply- and temperature-stable.

To achieve the difficult performance objectives, a proprietary circuit form—the X-AMP®—has been developed. Each channel of the X-AMP comprises a variable attenuator of 0 dB to -42.14 dB followed by a high speed fixed gain amplifier. In this way, the amplifier never has to cope with large inputs, and can benefit from the use of negative feedback to precisely define the gain and dynamics. The attenuator is realized as a seven-stage R-2R ladder network having an input resistance of 100Ω , laser-trimmed to $\pm 2\%$. The attenuation between tap points is 6.02dB ; the gain-control circuit provides continuous interpolation between these taps. The resulting control function is linear in dB.

Dual, Low Noise, Wideband
Variable Gain Amplifiers

AD600/AD602*

FUNCTIONAL BLOCK DIAGRAM

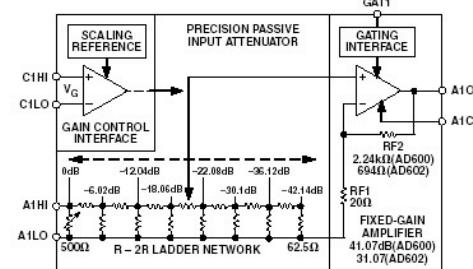

The gain-control interfaces are fully differential, providing an input resistance of $\sim 15 \text{ M}\Omega$ and a scale factor of 32 dB/V (that is, $31.25 \text{ mV}/\text{dB}$) defined by an internal voltage reference. The response time of this interface is less than $1 \mu\text{s}$. Each channel also has an independent gating facility that optionally blocks signal transmission and sets the dc output level to within a few millivolts of the output ground. The gating control input is TTL and CMOS compatible.


The maximum gain of the AD600 is 41.07 dB, and that of the AD602 is 31.07 dB; the -3 dB bandwidth of both models is nominally 35 MHz, essentially independent of the gain. The signal-to-noise ratio (SNR) for a 1 V rms output and a 1 MHz noise bandwidth is typically 76 dB for the AD600 and 86 dB for the AD602. The amplitude response is flat within $\pm 0.5 \text{ dB}$ from 100 kHz to 10 MHz; over this frequency range the group delay varies by less than $\pm 2 \text{ ns}$ at all gain settings.

Each amplifier channel can drive 100Ω load impedances with low distortion. For example, the peak specified output is $\pm 2.5 \text{ V}$ minimum into a 500Ω load, or $\pm 1 \text{ V}$ into a 100Ω load. For a 200Ω load in shunt with 5 pF, the total harmonic distortion for a $\pm 1 \text{ V}$ sinusoidal output at 10 MHz is typically -60 dBc .

The AD600J and AD602J are specified for operation from 0°C to 70°C , and are available in both 16-lead plastic DIP (N) and 16-lead SOIC (R). The AD600A and AD602A are specified for operation from -40°C to $+85^\circ\text{C}$ and are available in both 16-lead cerdip (Q) and 16-lead SOIC (R).

The AD600S and AD602S are specified for operation from -55°C to $+125^\circ\text{C}$ and are available in a 16-lead cerdip (Q) package and are MIL-STD-883 compliant. The AD600S and AD602S are also available under DESC SMD 5962-94572.

OTA's (LM3080, LM13700)

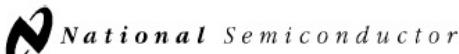

February 1995

LM3080 Operational Transconductance Amplifier

General Description


The LM3080 is a programmable transconductance block intended to fulfill a wide variety of variable gain applications. The LM3080 has differential inputs and high impedance push-pull outputs. The device has high input impedance and its transconductance (g_m) is directly proportional to the amplifier bias current (I_{ABC}).

High slew rate together with programmable gain make the LM3080 an ideal choice for variable gain applications such as sample and hold, multiplexing, filtering, and multiplying. The LM3080N and LM3080AN are guaranteed from 0°C to +70°C.


Features

- Slew rate (unity gain compensated): 50 V/ μ s
- Fully adjustable gain: 0 to $g_m \cdot R_L$ limit
- Extended g_m linearity: 3 decades
- Flexible supply voltage range: $\pm 2V$ to $\pm 18V$
- Adjustable power consumption

Schematic and Connection Diagrams

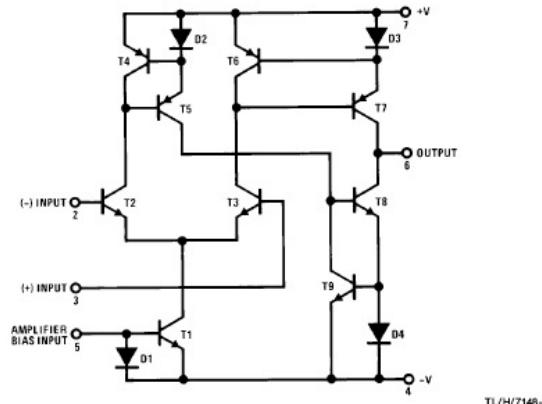

Dual-In-Line Package

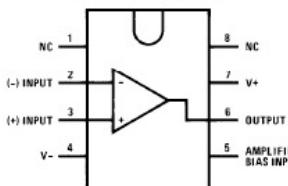

Current Output

Need Transimpedance Amp

Order Number LM3080AN, LM3080M or LM3080N
See NS Package Number M08A or N08E



LM13700

Dual Operational Transconductance Amplifiers with Linearizing Diodes and Buffers

General Description

The LM13700 series consists of two current controlled transconductance amplifiers, each with differential inputs and a push-pull output. The two amplifiers share common supply voltages and have independent bias currents. Linearizing diodes are provided at the inputs to reduce distortion and allow higher input levels. The result is a 10 dB signal-to-noise improvement referenced to 0.5 percent THD. High impedance buffers are provided which are especially designed for audio applications.

The output buffers of the LM13700 differ from those of the LM13600 in that their input bias currents (and hence their output DC levels) are independent of I_{ABC} . This may result in performance superior to that of the LM13600 in audio applications.


Features

- g_m adjustable over 6 decades
- Excellent g_m linearity
- Excellent matching between amplifiers
- Linearizing diodes
- High impedance buffers
- High output signal-to-noise ratio


Applications

- Current-controlled amplifiers
- Current-controlled impedances
- Current-controlled filters
- Current-controlled oscillators
- Multiplexers
- Timers
- Sample-and-hold circuits

Dual-In-Line and Small Outline Packages

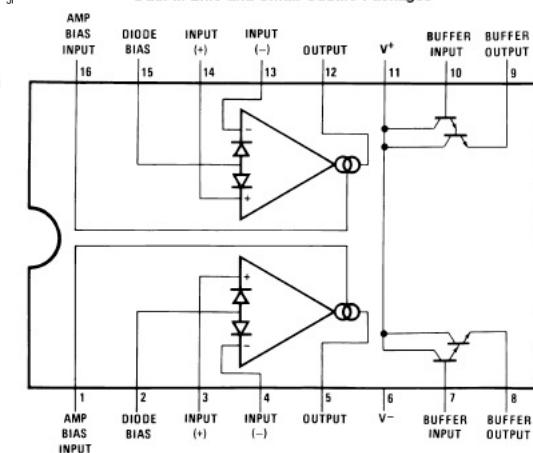

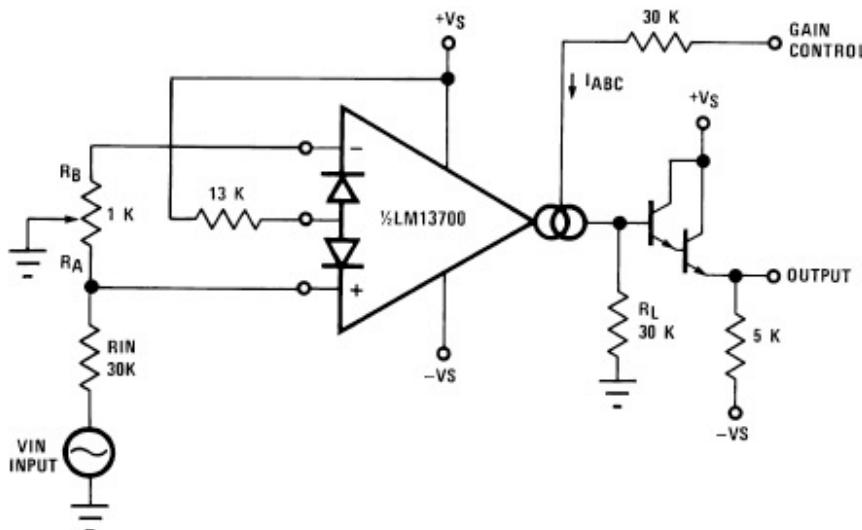Top View
Order Number LM13700M, LM13700MX or LM13700N
See NS Package Number M16A or N16A



VCA Arrays



Low Cost Quad Voltage Controlled Amplifier

SSM2164

FEATURES

- Four High Performance VCAs in a Single Package
- 0.02% THD
- No External Trimming
- 120 dB Gain Range
- 0.07 dB Gain Matching (Unity Gain)
- Class A or AB Operation

APPLICATIONS

- Remote, Automatic, or Computer Volume Controls
- Automotive Volume/Balance/Faders
- Audio Mixers
- Compressor/Limiters/Compandors
- Noise Reduction Systems
- Automatic Gain Controls
- Voltage Controlled Filters
- Spatial Sound Processors
- Effects Processors

GENERAL DESCRIPTION


The SSM2164 contains four independent voltage controlled amplifiers (VCAs) in a single package. High performance (100 dB dynamic range, 0.02% THD) is provided at a very low cost-per-VCA, resulting in excellent value for cost sensitive gain control applications. Each VCA offers current input and output for maximum design flexibility, and a ground referenced -33 mV/dB control port.

All channels are closely matched to within 0.07 dB at unity gain, and 0.24 dB at 40 dB of attenuation. A 120 dB gain range is possible.

A single resistor tailors operation between full Class A and AB modes. The pinout allows upgrading of SSM2024 designs with minimal additional circuitry.

The SSM2164 will operate over a wide supply voltage range of ± 4 V to ± 18 V. Available in 16-pin P-DIP and SOIC packages, the device is guaranteed for operation over the extended industrial temperature range of -40°C to $+85^{\circ}\text{C}$.

FUNCTIONAL BLOCK DIAGRAM

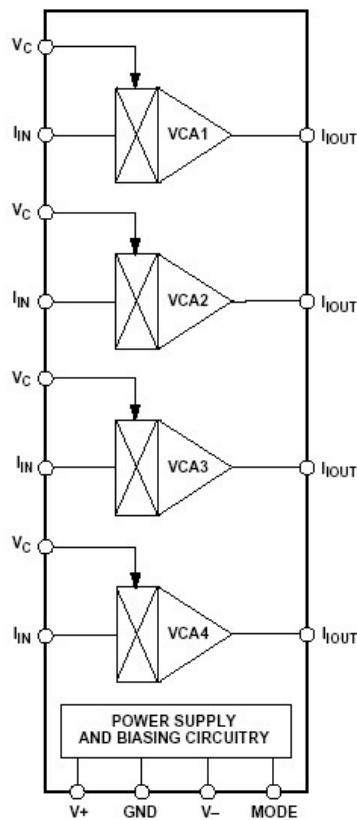

Analog Multipliers (4-Quadrant)



Low Cost
Analog Multiplier

AD633

FEATURES

- 4-Quadrant Multiplication
- Low Cost 8-Lead Package
- Complete – No External Components Required
- Laser-Trimmed Accuracy and Stability
- Total Error within 2% of FS
- Differential High Impedance X and Y Inputs
- High Impedance Unity-Gain Summing Input
- Laser-Trimmed 10 V Scaling Reference

APPLICATIONS

- Multiplication, Division, Squaring
- Modulation/Demodulation, Phase Detection
- Voltage Controlled Amplifiers/Attenuators/Filters

PRODUCT DESCRIPTION

The AD633 is a functionally complete, four-quadrant, analog multiplier. It includes high impedance, differential X and Y inputs and a high impedance summing input (Z). The low impedance output voltage is a nominal 10 V full scale provided by a buried Zener. The AD633 is the first product to offer these features in modestly priced 8-lead plastic DIP and SOIC packages.


The AD633 is laser calibrated to a guaranteed total accuracy of 2% of full scale. Nonlinearity for the Y input is typically less than 0.1% and noise referred to the output is typically less than 100 μV rms in a 10 Hz to 10 kHz bandwidth. A 1 MHz bandwidth, 20 V/ μs slew rate, and the ability to drive capacitive loads make the AD633 useful in a wide variety of applications where simplicity and cost are key concerns.

The AD633's versatility is not compromised by its simplicity. The Z-input provides access to the output buffer amplifier, enabling the user to sum the outputs of two or more multipliers, increase the multiplier gain, convert the output voltage to a current, and configure a variety of applications.


The AD633 is available in an 8-lead plastic DIP package (N) and 8-lead SOIC (R). It is specified to operate over the 0°C to 70°C commercial temperature range (J Grade) or the -40°C to +85°C industrial temperature range (A Grade).

CONNECTION DIAGRAMS

8-Lead Plastic DIP (N) Package

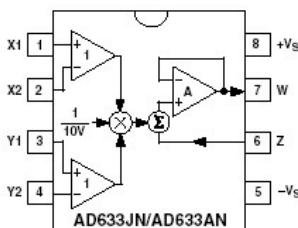

8-Lead Plastic SOIC (RN-8) Package

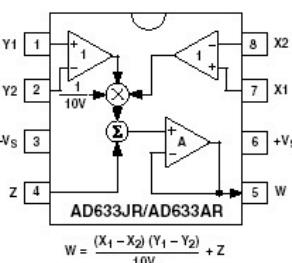

PRODUCT HIGHLIGHTS

1. The AD633 is a complete four-quadrant multiplier offered in low cost 8-lead plastic packages. The result is a product that is cost effective and easy to apply.
2. No external components or expensive user calibration are required to apply the AD633.
3. Monolithic construction and laser calibration make the device stable and reliable.
4. High ($10 \text{ M}\Omega$) input resistances make signal source loading negligible.
5. Power supply voltages can range from $\pm 8 \text{ V}$ to $\pm 18 \text{ V}$. The internal scaling voltage is generated by a stable Zener diode; multiplier accuracy is essentially supply insensitive.

4 Quadrant means:
Multiplying by
negative values
(negative voltages)
inverts the output.
Either input can go
negative.

VCA's are 2 Quadrant
devices – the control
input can't go
negative, although the
signal input can.